 


# Fault Simulation


- **Introduction**
- **Fault simulation techniques**
  - ◆ **Serial fault simulation**
  - ◆ **Parallel fault simulation (1965)**
  - ◆ **PPSFP (1985)**
  - ◆ **Deductive fault simulation (1972)**
  - ◆ **Concurrent fault simulation (1974) \***
  - ◆ **Differential fault simulation (1989)**
- **Alternatives to fault simulation**
- **Issues of fault simulation**
- **Concluding remarks**



**\* Based on textbook  
“VLSI Test Principles and Architectures”  
by Wang, Wu, and Wen**
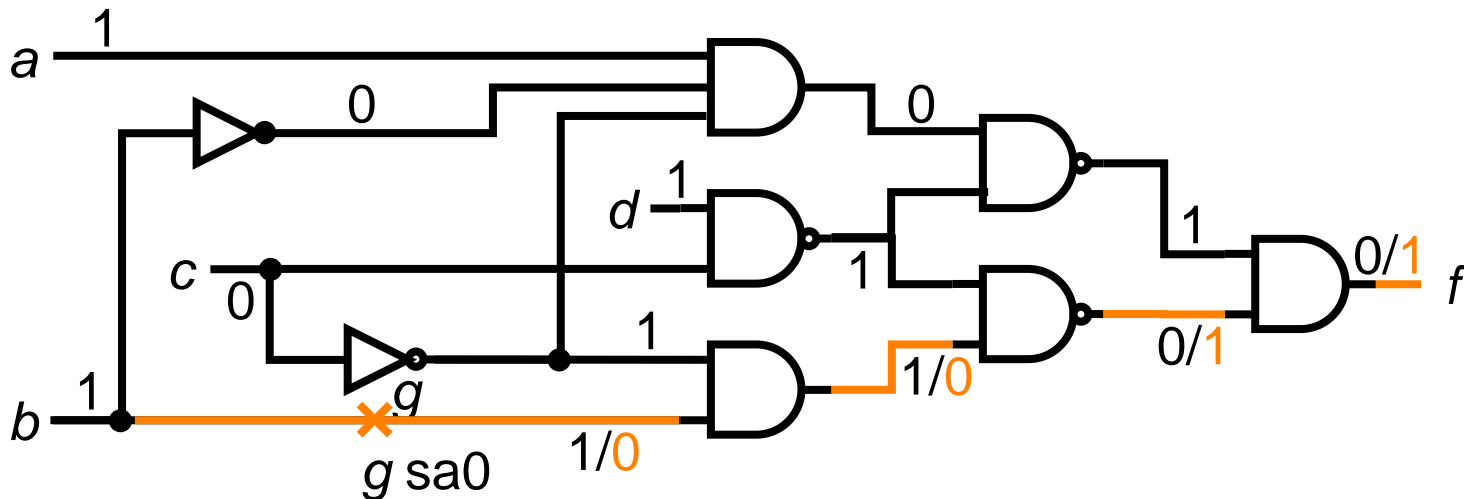
# Concurrent Fault Simulation [Ulrich 74]


- Observation
  - ♦ Fault activity is often sparse both in time and space
  - ♦ Example: *g sa0* fault only affects lower part of circuit
- Idea: can we just simulate parts of faulty circuit that **differs** from good circuit?



**Concurrent fault sim. Is  
event-driven sim. with good/bad events together**

 
# Bad Gate

- Every **good gate** has a list of **bad gates**
- Bad-gate
  - ♦ Represents fault effect of a fault
  - ♦ At least **one gate input or output differs** from its corresponding good-gate if the fault is present
  - ♦ A bad gate is denoted by
    - \* Fault: a stuck-at 0 , b stuck-at 0
    - \* Faulty input value, faulty output value



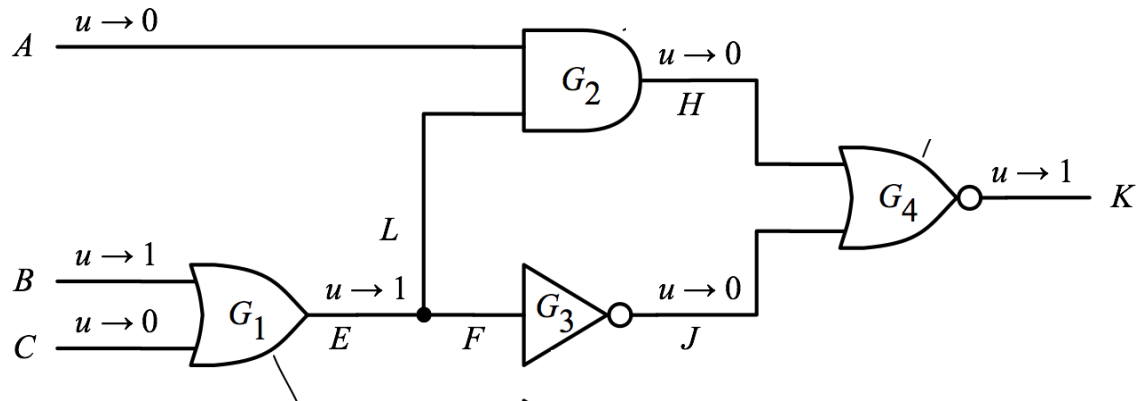
# Example ( $P_1$ )

- Fault-free simulation, Pattern  $P_1 = 010$
- Event-driven simulation
  - **Good events** are events occur in a good circuit



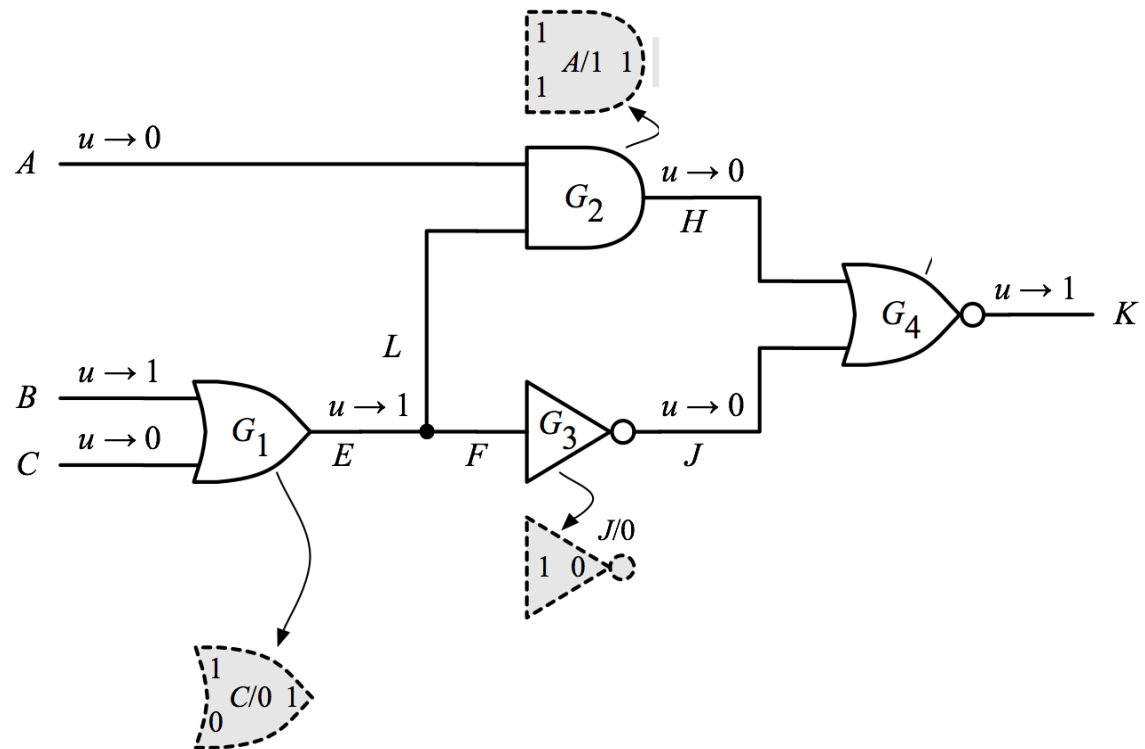
# Example ( $P_1$ )

- Consider only three faults:  $A/1$ ,  $J/0$ ,  $C/0$  (WWW Fig 3.30)
  - Good gates in white:  $G_1 \sim G_4$
  - Bad gates in gray:  $A/1$ ,  $J/0$ ,  $C/0$
- A bad gate is **invisible** if its faulty output same as good values
  - $C/0$   $J/0$  are invisible
- A bad gate is **visible** if its faulty output different from good values
  - $A/1$  is visible



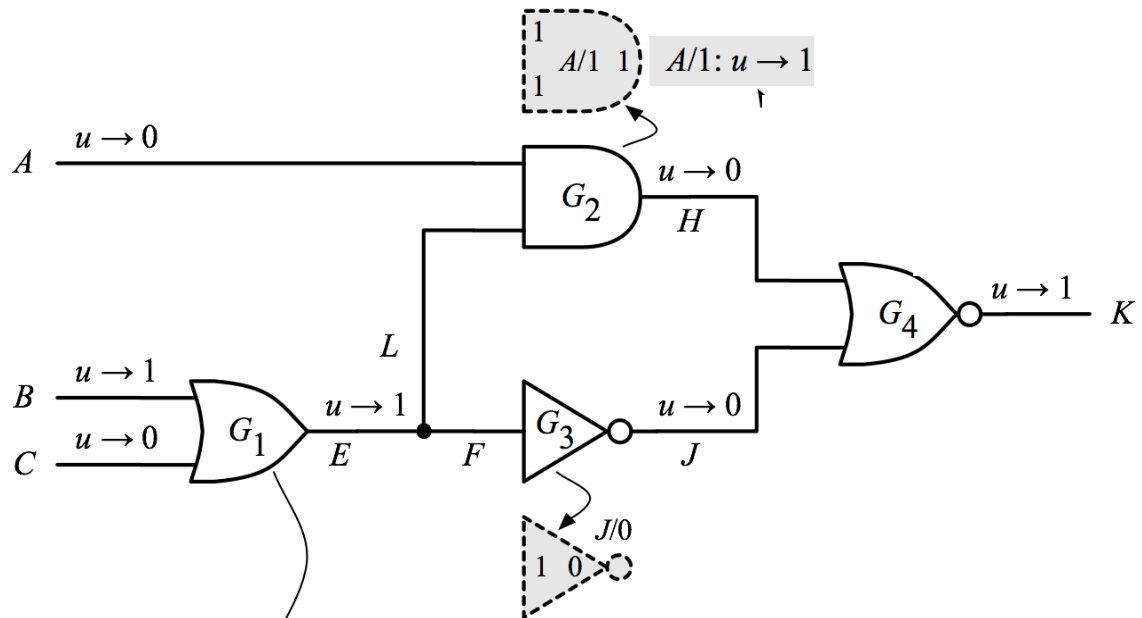
# Bad Events

- **Bad events:** Events in faulty circuit, and **different** from good events
- Good events activate both good-gates and bad-gates for evaluation
- Bad events only activate bad-gates of same fault for evaluation
- Only events of visible bad gates will be propagated
  - ♦ Invisible bad gates will not trigger any bad event
- Example:
  - ♦ Good events in white:  $A \rightarrow 0$ ,  $H \rightarrow 0$ , ...
  - ♦ Bad events in gray
    - \*  $G_2$   $A/1: u \rightarrow 1$


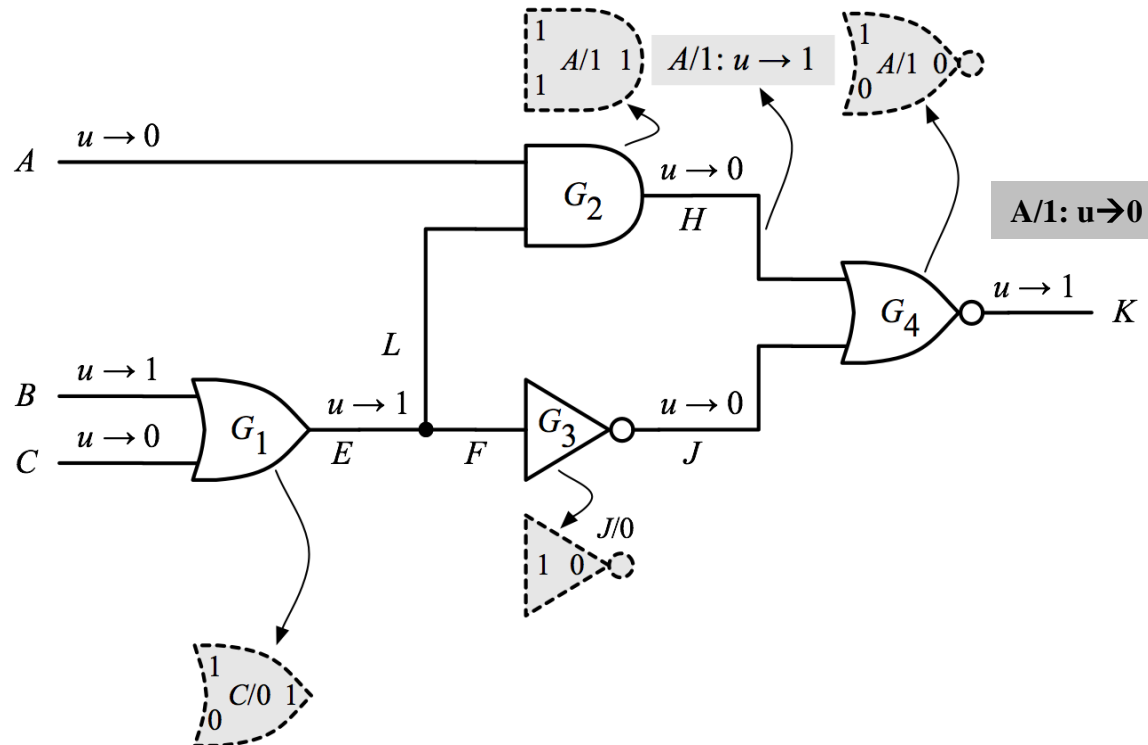
# Example ( $P_1$ )


- Bad gate **diverges** from its good gate if its faulty I/O values are different from good values
- Example:
  - ♦ Bad gate ( $G_4$   $A/1$ ) *diverges* from its good gate
  - ♦  $A/1$  is detected by  $P_1$


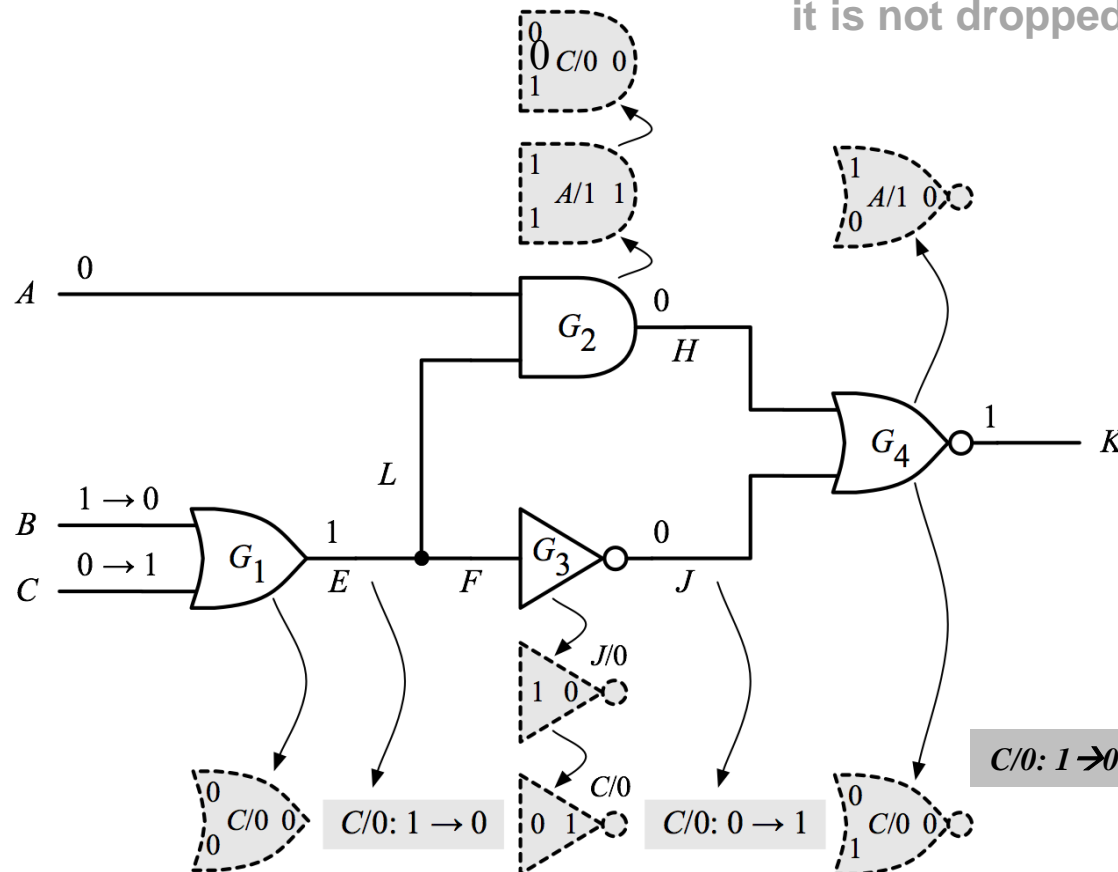
# Example ( $P_2$ )

- $P_1 \rightarrow P_2$  010  $\rightarrow$  001; Note: **no other good event inside circuit**
- **C/0** becomes newly visible
- **A/1, C/0** detected by  $P_2$


Although A/1 has been detected, it is not dropped for demo purpose





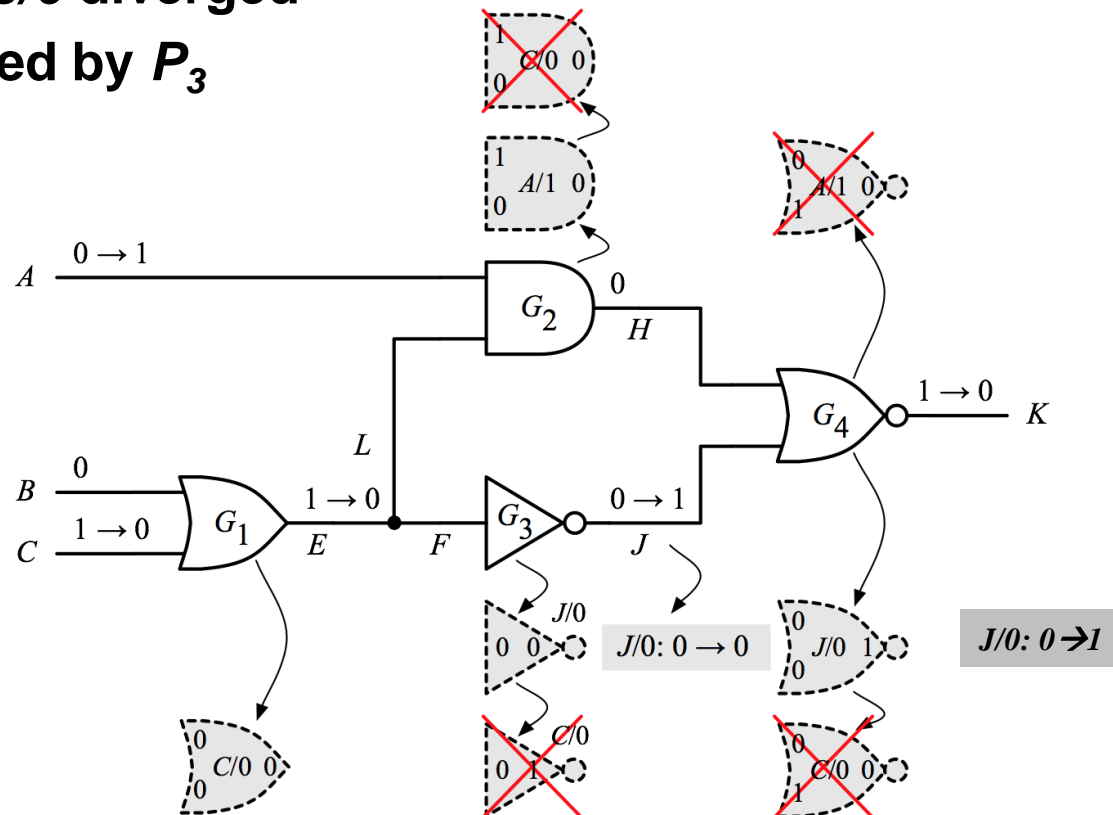
# Example ( $P_3$ )

- $P_2 \rightarrow P_3$  001  $\rightarrow$  100
- Bad gate **converges** (disappear) to its good gate if its faulty I/O values become same as good values
- Example : Bad gates A/1 C/0 converged
  - ♦ Bad gate J/0 diverged
  - ♦ J/0 detected by  $P_3$



# Concurrent Fault Sim. Flow

- WWW Fig 3.33

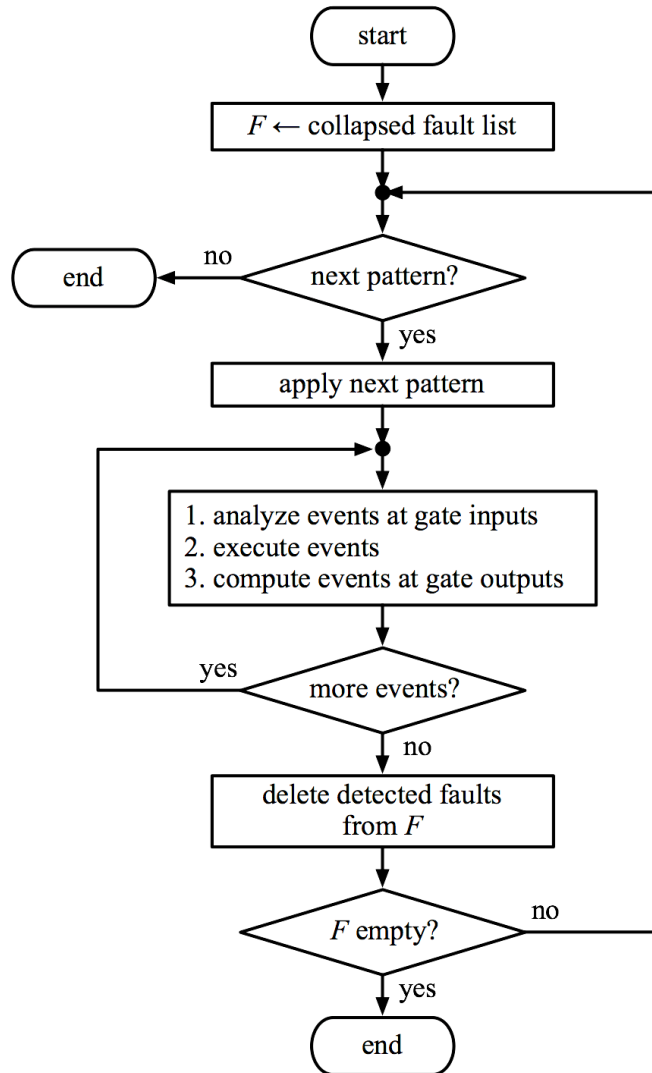

# Concurrent Fault Simulation Summary

- **Advantages**
  - ◆ Even faster than deductive fault simulation
  - ◆ Delay fault can be supported
  - ◆ Sequential fault simulation can be supported
- **Disadvantage**
  - ◆ Difficulty in memory management
    - \* Memory requirement not predictable

# FFT

- Q1: In P2, why no bad events there?
- Q2: Why delay fault is supported?
- Q3: Why sequential circuit ok?

Q: why no bad events here?

