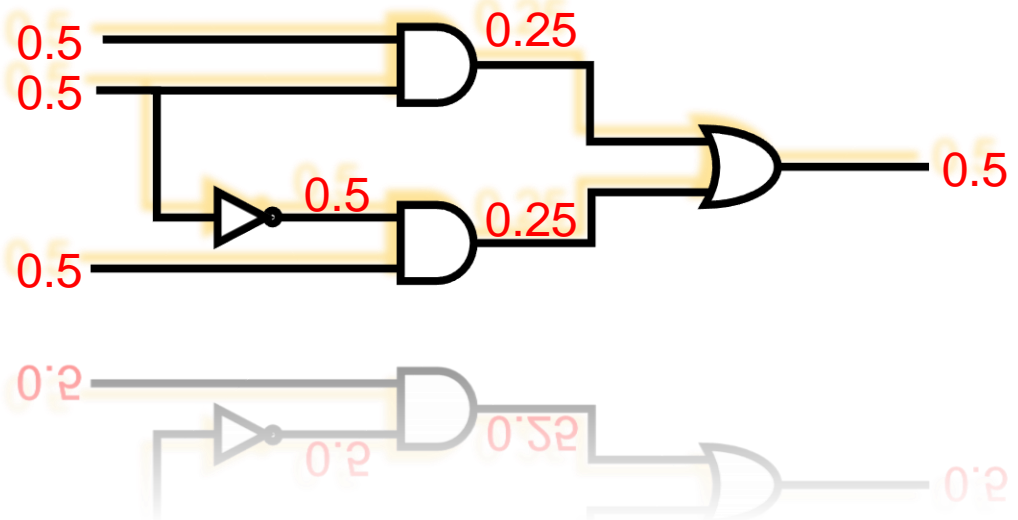


Testability Measure

- Introduction
- **SCOAP**
 - ♦ Combinational
 - ♦ Sequential
- COP
- High-level testability measures








Sequential SCOAP Measures






- **Sequential controllability: $SC^0(N)$, $SC^1(N)$**
 - ♦ Minimum number of **FF assignments** (number of clock cycles) required to control 0 or 1 on node N
 - ♦ **smaller** number means **easier** to control
- **Sequential observability: $SO(N)$**
 - ♦ Minimum number of **FF assignments** required to propagate logical value on node N to a primary output
- **NOTE: assume no scan**
 - ♦ Can only control PI, observe PO
 - ♦ Can **NOT** control FF, can **NOT** observe FF

**Sequential SCOAP Measures
of Clock Cycles Needed**

SC⁰(N) and SC¹(N)

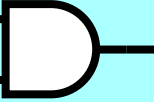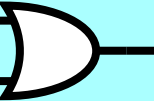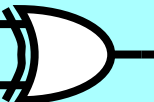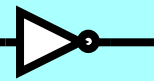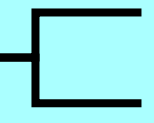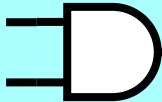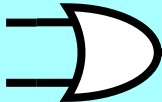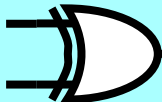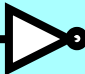
	SC ⁰ (y)	SC ¹ (y)
Primary inputs	0 (not 1)	0
x_1 x_2  y	$\min[\text{SC}^0(x_1), \text{SC}^0(x_2)]$ +1	$\text{SC}^1(x_1) + \text{SC}^1(x_2)$
x_1 x_2  y	$\text{SC}^0(x_1) + \text{SC}^0(x_2)$	$\min[\text{SC}^1(x_1), \text{SC}^1(x_2)]$
x_1 x_2  y	$\min[\text{SC}^0(x_1) + \text{SC}^0(x_2), \text{SC}^1(x_1) + \text{SC}^1(x_2)]$	$\min[\text{SC}^0(x_1) + \text{SC}^1(x_2), \text{SC}^1(x_1) + \text{SC}^0(x_2)]$
x  y	$\text{SC}^1(x)$	$\text{SC}^0(x)$
x_1  y_1 y_2	$\text{SC}^0(y_1) = \text{SC}^0(y_2) = \text{SC}^0(x_1)$	$\text{SC}^1(y_1) = \text{SC}^1(y_2) = \text{SC}^1(x_1)$

SO(N)

	SO(x_1)
Primary outputs	0
x_1 x_2  y	SO(y) + SC ¹ (x_2) X
x_1 x_2  y	SO(y) + SC ⁰ (x_2)
x_1 x_2  y	SO(y) + min[SC ⁰ (x_2), SC ¹ (x_2)]
x_1  y	SO(y)
x_1  y_1 y_2	min[SO(y_1), SO(y_2)]

Flip-Flop (Controllability)

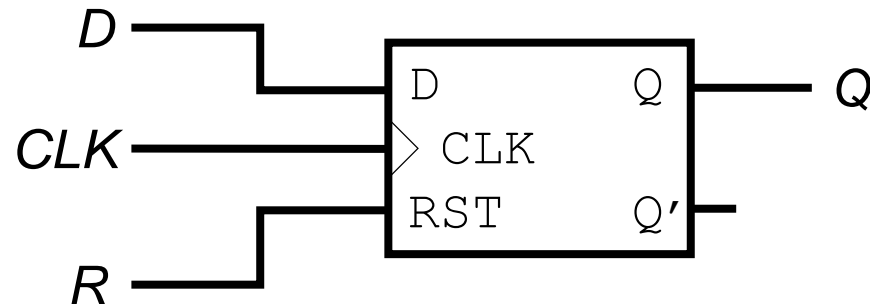
- Positive edge triggered, asynchronous reset



$$\begin{aligned} CC^1(Q) &= CC^1(D) + CC^1(CLK) + CC^0(CLK) + CC^0(R) \\ SC^1(Q) &= SC^1(D) + SC^1(CLK) + SC^0(CLK) + SC^0(R) + 1 \end{aligned}$$

$$\begin{aligned} CC^0(Q) &= \min[CC^1(R), \\ &\quad CC^0(D) + CC^1(CLK) + CC^0(CLK) + CC^0(R)] \\ SC^0(Q) &= \min[SC^1(R), \\ &\quad SC^0(D) + SC^1(CLK) + SC^0(CLK) + SC^0(R)] + 1 \end{aligned}$$

Flip-Flop (Observability)

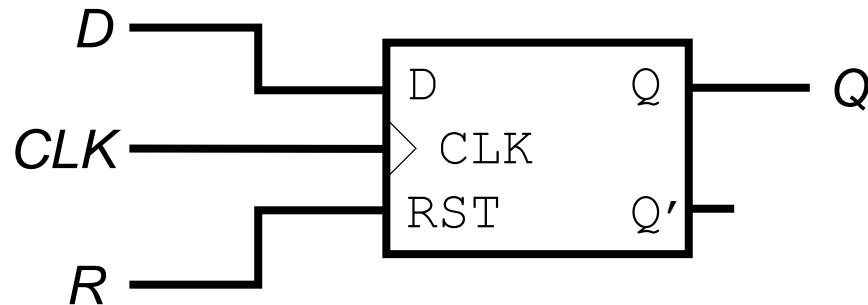


$$\begin{aligned} CO(D) &= CO(Q) + CC^1(CLK) + CC^0(CLK) + CC^0(R) \\ SO(D) &= SO(Q) + SC^1(CLK) + SC^0(CLK) + SC^0(R) + 1 \end{aligned}$$


Seq. SCOAP Computation Alg.

- Computation of SC, SO is similar to CC, CO
 - ♦ but require *iterations* for controllability to converge



Controllability:

1. For all PI's, set $CC^0 = CC^1 = 1$ and $SC^0 = SC^1 = 0$
2. For all other nodes, set $CC^0 = CC^1 = \infty$ and $SC^0 = SC^1 = \infty$
3. Propagate controllability from PI's to PO's 
Iterate until numbers stabilize.

Observability:

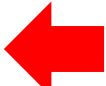
1. For all PO's, set $CO = SO = 0$
2. For all other nodes, set $CO = SO = \infty$
3. Propagate observability from PO's to PI's 
(note: no iteration needed for CO/SO)

Controllability Computation - 1

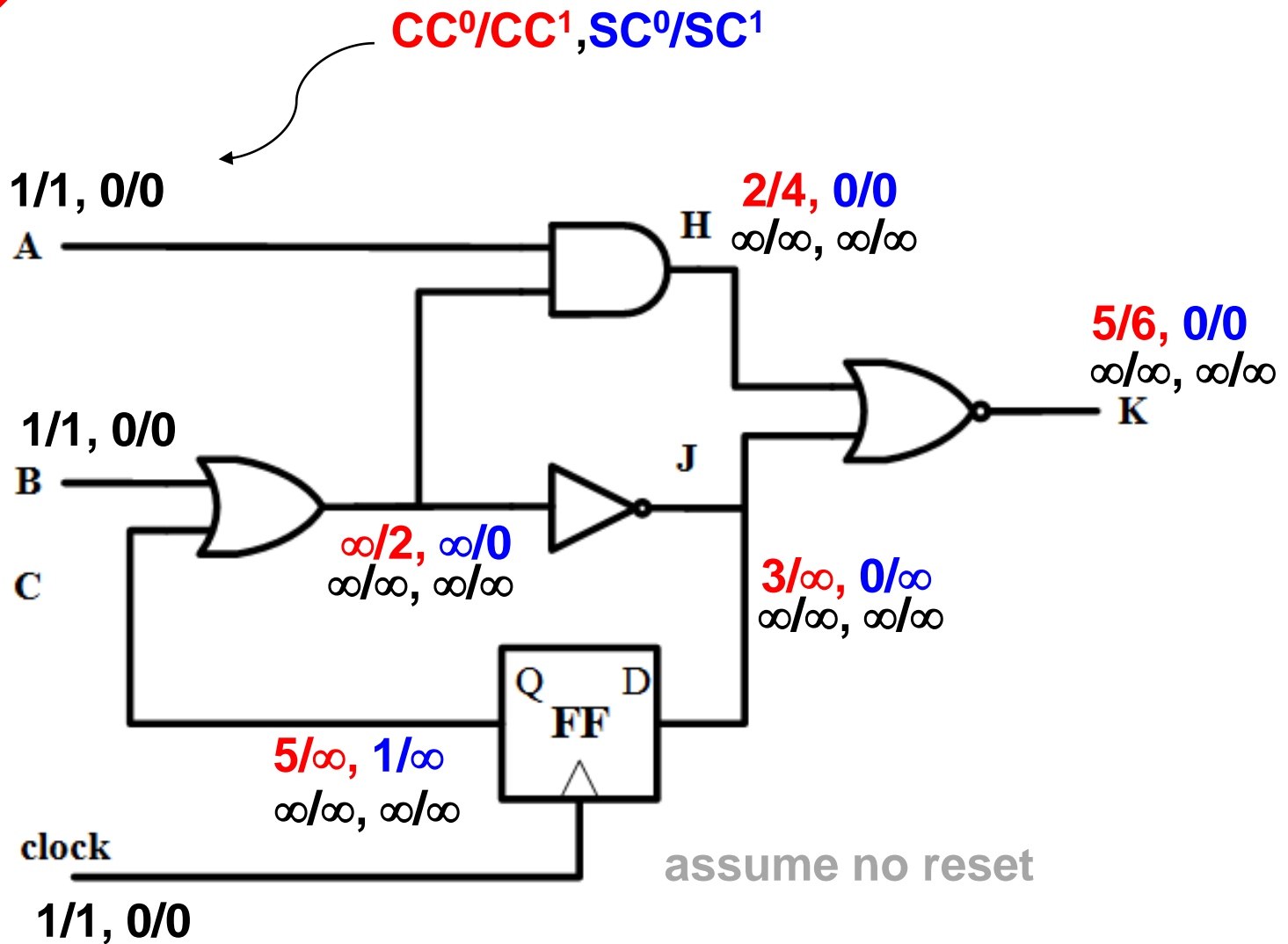
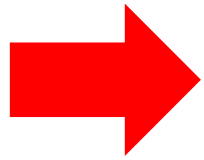


Quiz


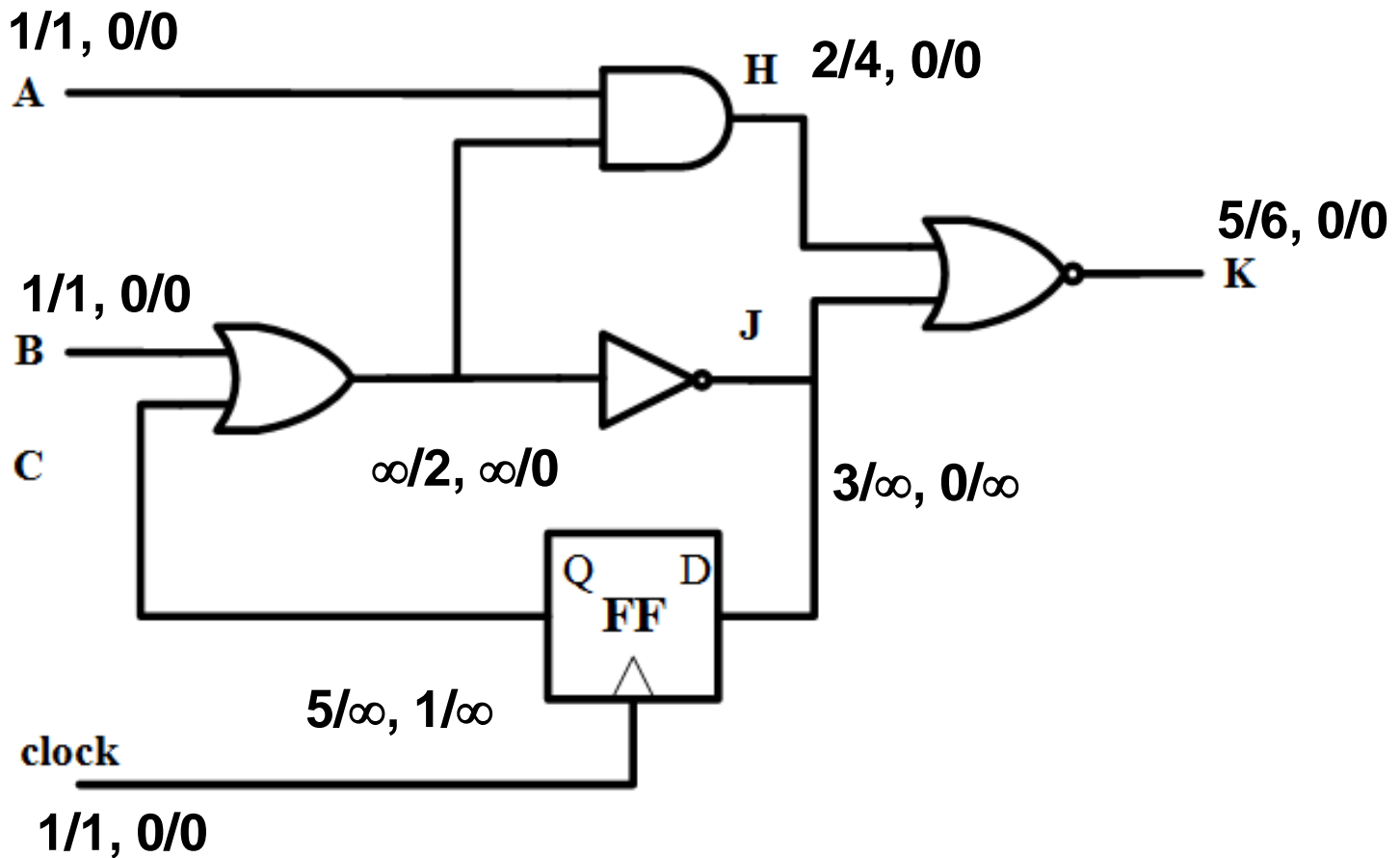
Q: Given numbers from the 1st iteration, please continue to calculate CC^0/CC^1 , SC^0/SC^1 in 2nd iteration.



Controllability Computation - 2

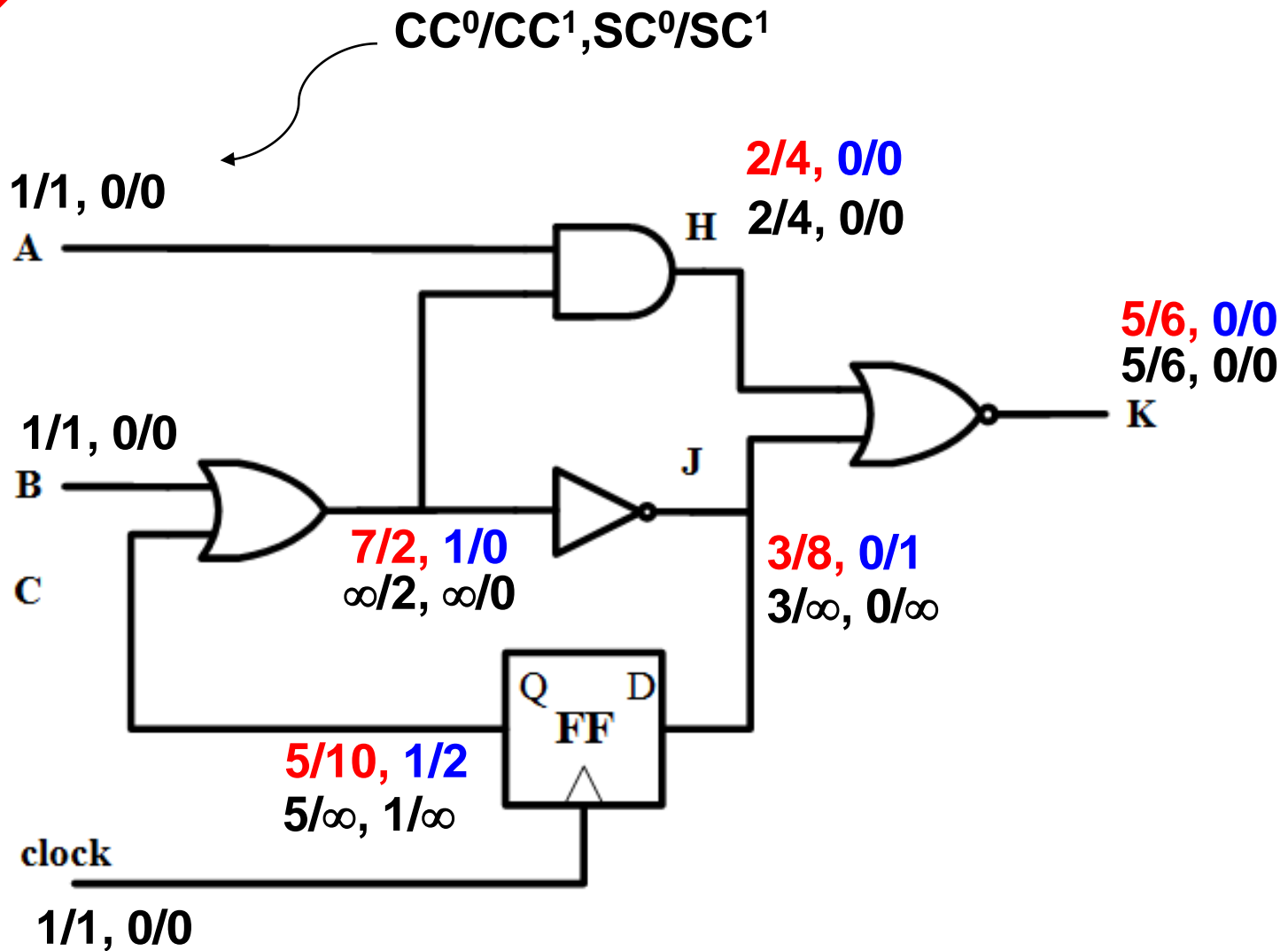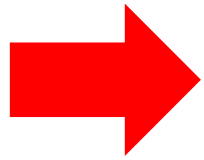


Controllability Computation - 3

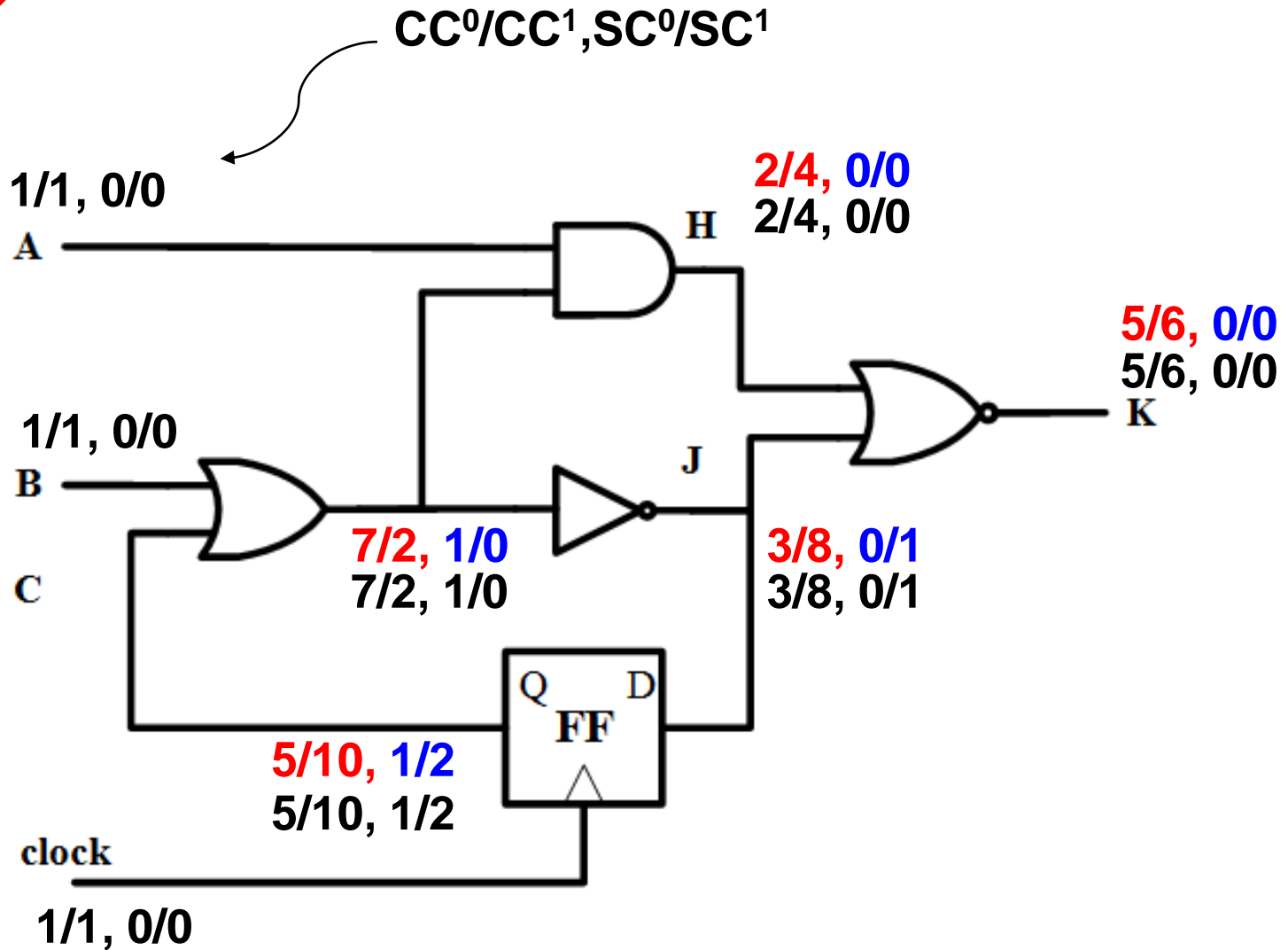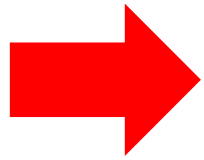


Quiz

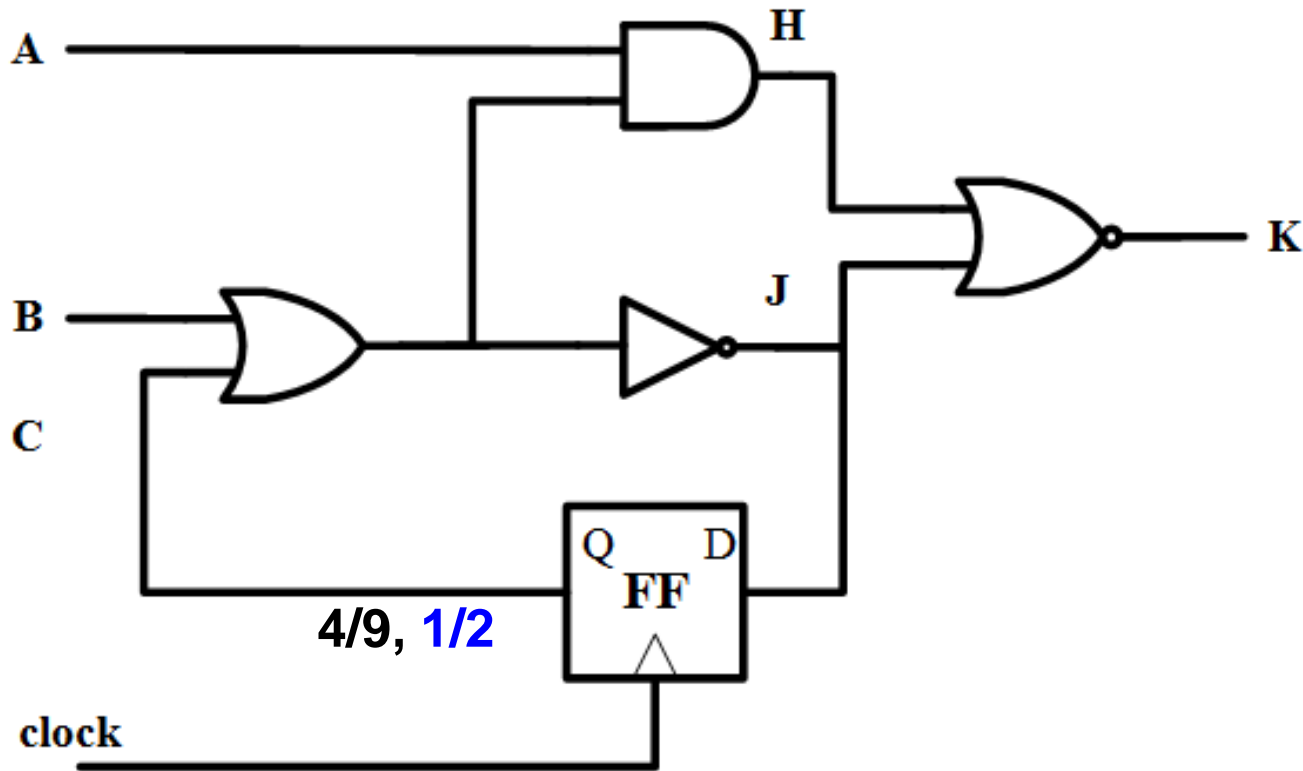Q1: Generate a sequence of test patterns to control C to 0?
Q2: Generate a sequence of test patterns to control C to 1?
(assume no scan. can only assign PI)





What Does $SC^1=2$ Mean?

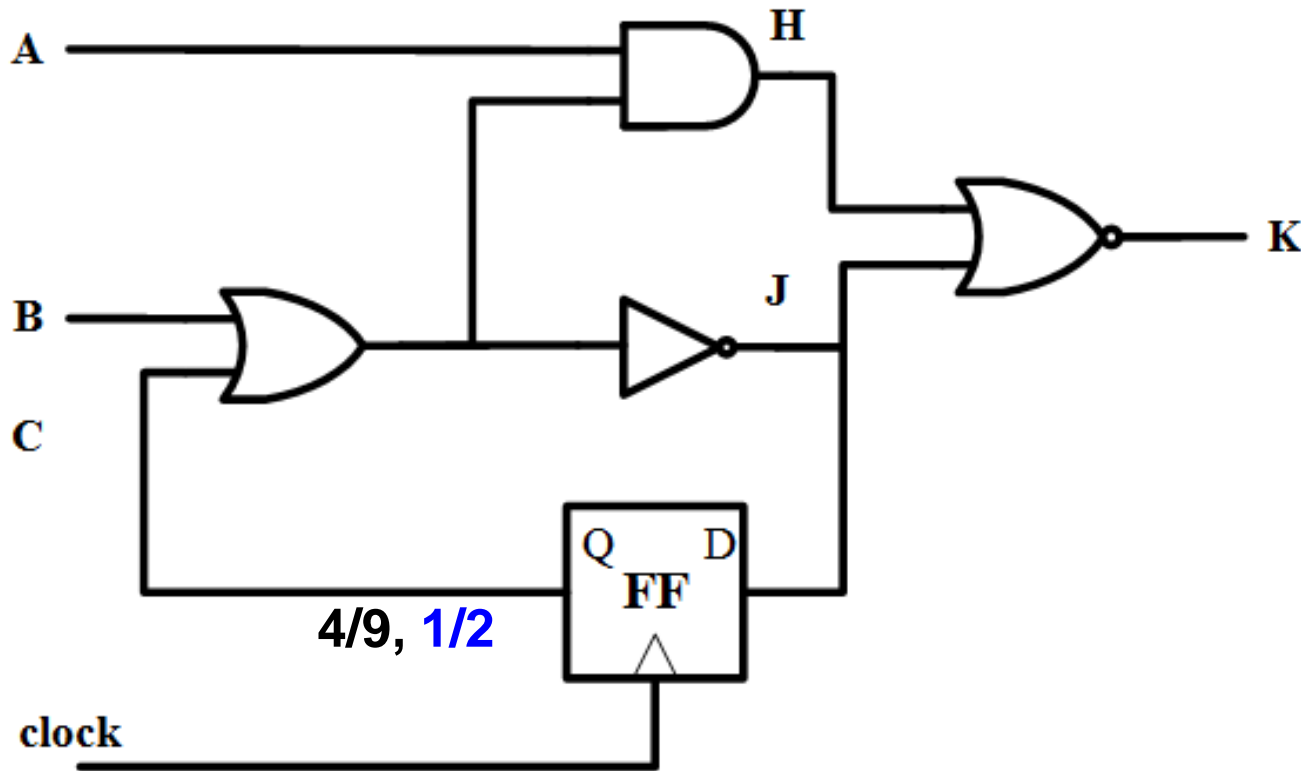- Control C to zero is easier. Assign $B=1$ and pulse **one** clock
- Control C to one is more difficult. Assign $B=1$ and $B=0$. **Two** clocks




Observability Computation

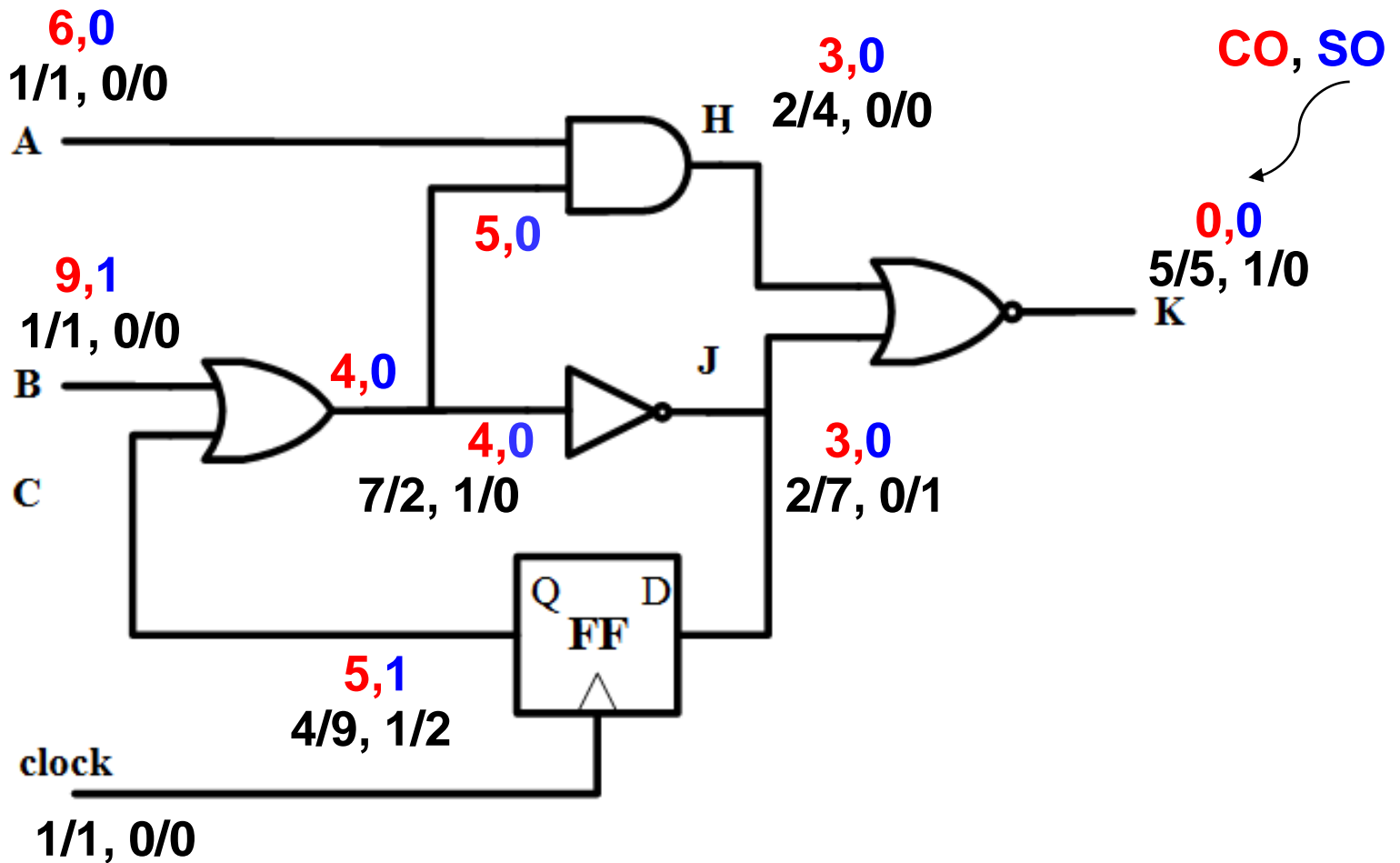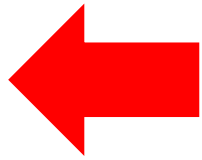


Quiz

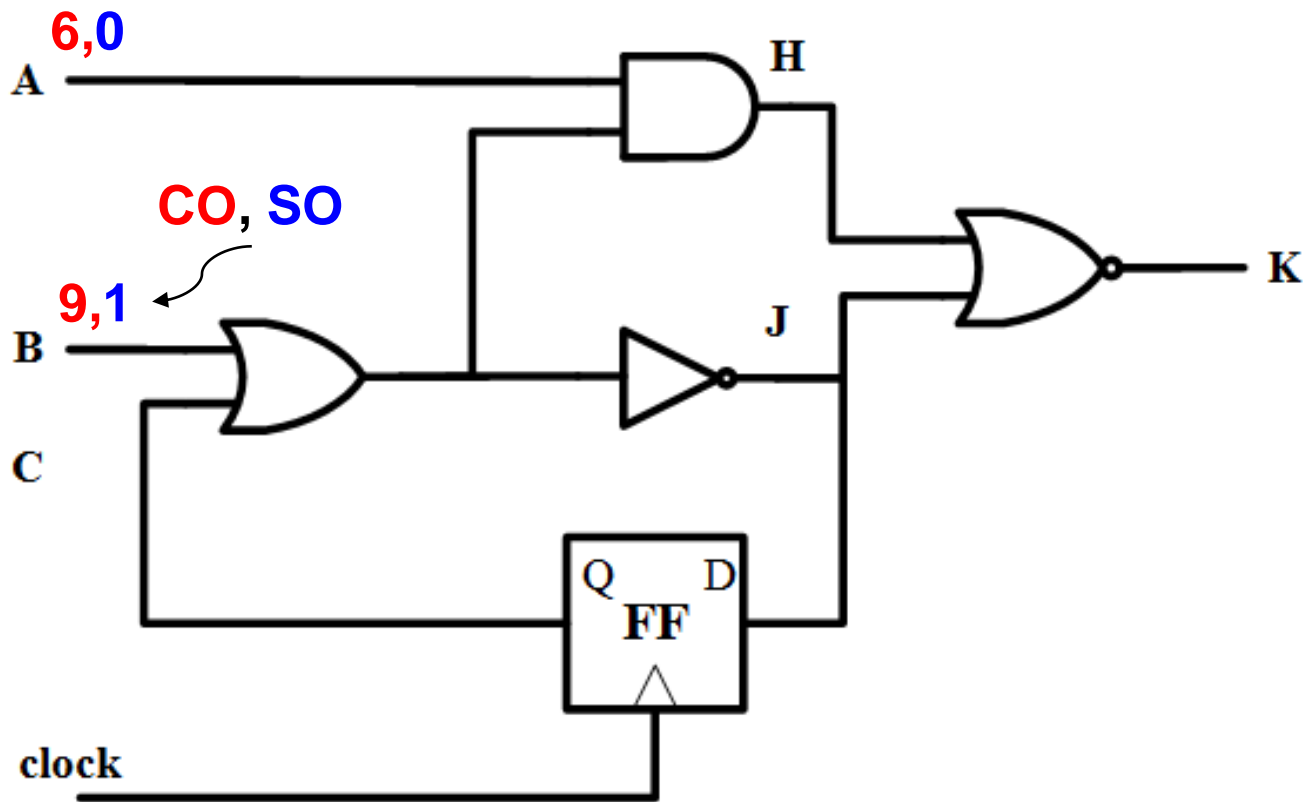Q1: Generate a sequence of test patterns to observe *A*?
Q2: Generate a sequence of test patterns to observe *B*?
(assume no scan. can only assign PI)




Summary

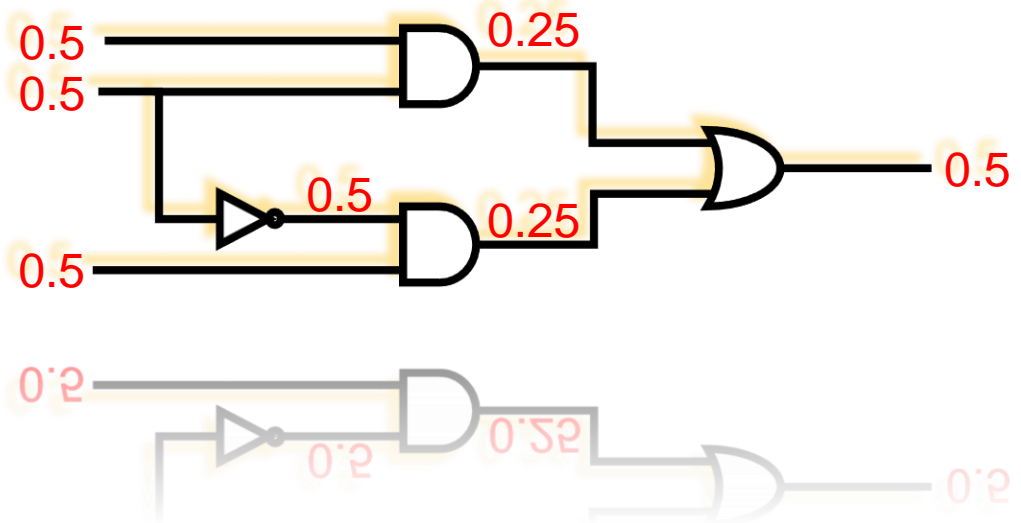- Sequential SCOAP
 - ♦ $SC^0 SC^1 = 0$ and 1 controllability; SO = observability
 - ♦ Measure **FF assignments** (or **clock cycles**) needed
 - ♦ **Smaller** means **easier**
 - ♦ No scan is allowed
- Requires **iterations** to compute SC



FFT

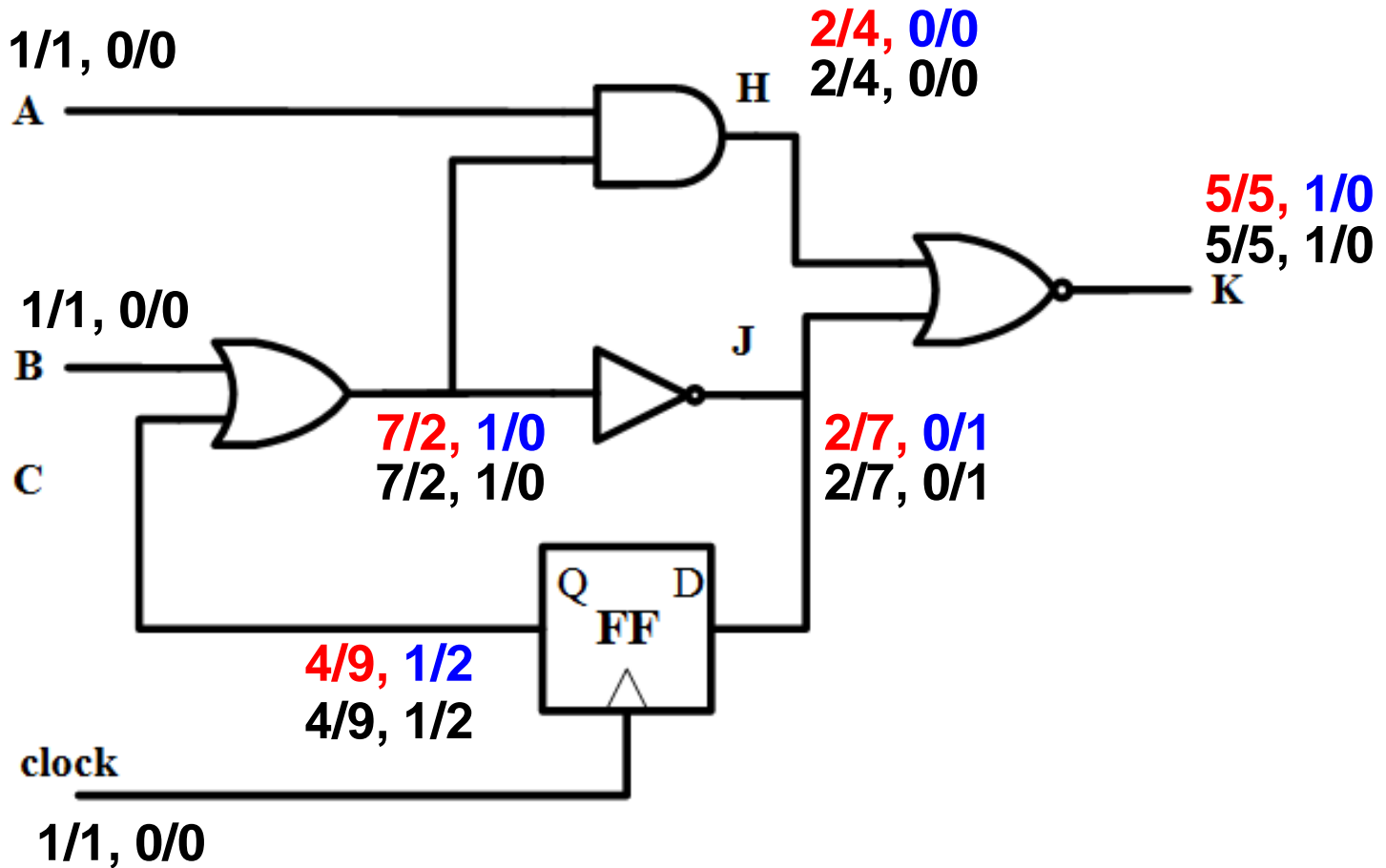- When does the algorithm fail to converge?



Computing Sequential SCOAP

- Computation of $SC^0(M)$, $SC^1(M)$, and $SO(M)$ is similar to
 - ♦ $CC^0(M)$, $CC^1(M)$, and $CO(M)$.
- Differences are
 - ① Increments sequential SCOAP by 1 only when signals propagate from **FF** inputs to Q, or backwards
 - ② May require *iterations* for controllability to converge