 



# Advanced Topics: ATPG

- Introduction
- Defect-based Testing
- **Advanced ATPG**
  - ◆ N-detect ATPG (Stanford 1995)
  - ◆ Cell-aware ATPG (Mentor 2009)
  - ◆ **Timing-aware ATPG (Mentor 2006)**
    - \* **Introduction**
    - \* **ATPG algorithm**
    - \* **Experimental Results**
  - ◆ Power-aware ATPG (KIT 2005)
- Conclusion


 
# ATPG Choose Short Path

- Review: PODEM chose **shortest** X-path to PO
  - (Video 7.5)



- Stanford Murphy Experiment [Tseng 01]
  - Some outputs do not fail on tester
  - Shorter path can result in **test escape**

**Short Paths are Fast  
But Not Good Quality**


Table 6: Failing Output Bits for Chip 2

Test Set	Failing Output Bits	
	Simulation	Tester
SSF Tool 2A, 1-detect	1,2,3,9	9
SSF Tool 2A, 2-detect	1,2,5,8	5
SSF Tool 3C, 1-detect	2,8	5,9
Tool 4C, 1-detect	1,5,9	5,9
Transition	1,2,5,9	5,9


Table 7: Failing Output Bits for Chip 5

Test Set	Failing Output Bits	
	Simulation	Tester
SSF Tool 2A, 1-detect	1,2,3,9	1,9
SSF Tool2A, 2-detect	1,2,5,8	1
SSF Tool 3C, 1-detect	2,8	1
Tool 4C, 1-detect	1,5,9	1
Transition	1,2,5,9	1,9

# Three Types of Paths and Clock Timing

 

Three types of paths through a fault.

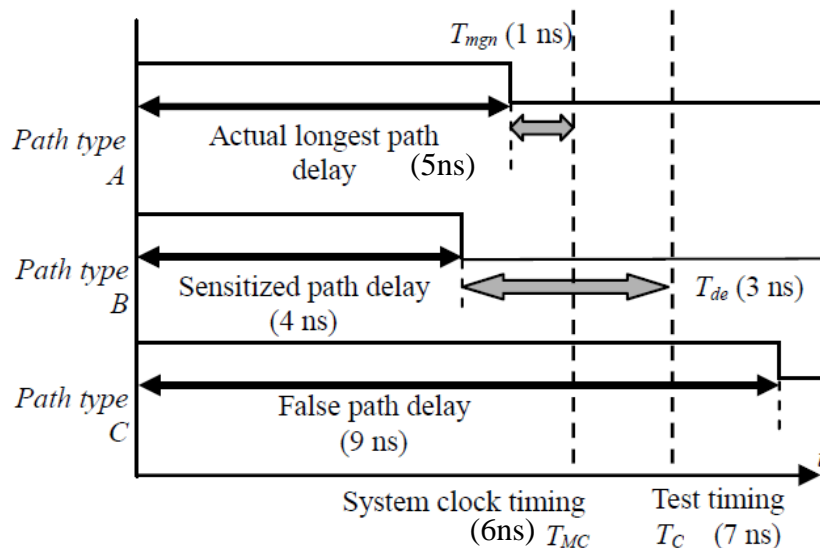

Timing relations for the three types of paths.

**Actual longest path** = Sensitizable longest path in this design.  
**Sensitized path** is **activated** and **propagated** by a test pattern.  
**False paths** do not need testing because **NOT sensitizable**, or **Functionally useless**


$T_{MC}$  = system clock timing, limited by **actual longest path**. Used in functional operation.  
 $T_C$  = test clock timing, limited by **tester**.  
 Typically,  $T_{MC} \leq T_{TC}$

$T_{mgn}$  = difference between **actual longest path** and **system clock**.  
 $T_{de}$  = difference between **sensitized path** and **test clock**.


**Good Test Sensitizes Long Paths but Not False Paths**
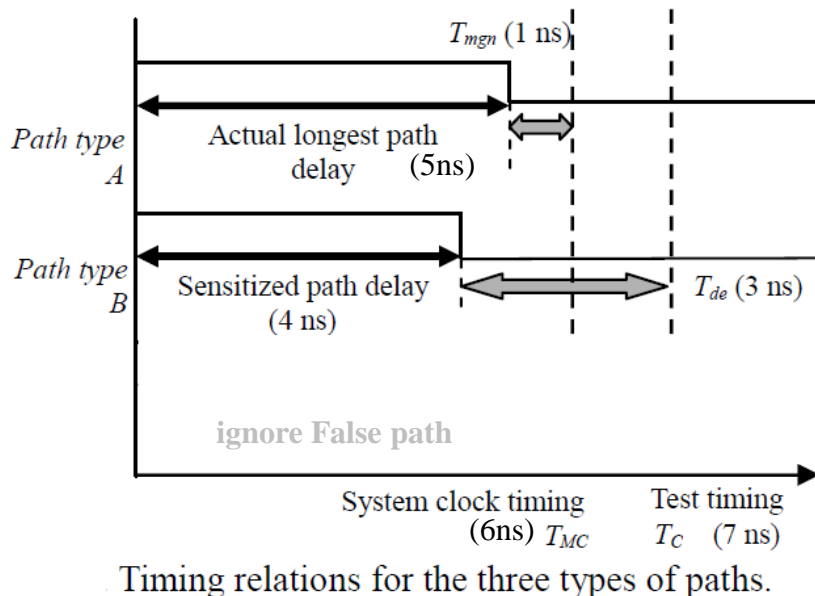
# Small Delay Defects (SDD) [Park 92][Sato 05]

- SDD = small delay defects **NOT** easily detected by slow tests
- Two solutions to reduce SDD
  - ♦ 1) Smaller  $T_{de}$ : **at-speed testing**  $T_{MC}=T_C$  (or faster than at-speed test  $T_{MC} > T_C$ )
  - ♦ 2) Longer sensitized path: **Timing-aware ATPG**



 
defect size ( $s$ ) and density  $F(s)$  distribution\*




**Timing-aware ATPG Improves DPM**
 
# Advanced Topics: ATPG

- Introduction
- Defect-based Testing
- **Advanced ATPG**
  - ◆ N-detect (Stanford 1995)
  - ◆ Cell-aware (Mentor 2009)
  - ◆ Timing-aware (**Mentor 2006**)
    - \* **Introduction**
    - \* **ATPG Algorithm**
    - \* **Experimental Results**
  - ◆ Power-aware (KIT 2005)
- Conclusion



# Timing-Aware ATPG\* [Mentor/Lin 06]

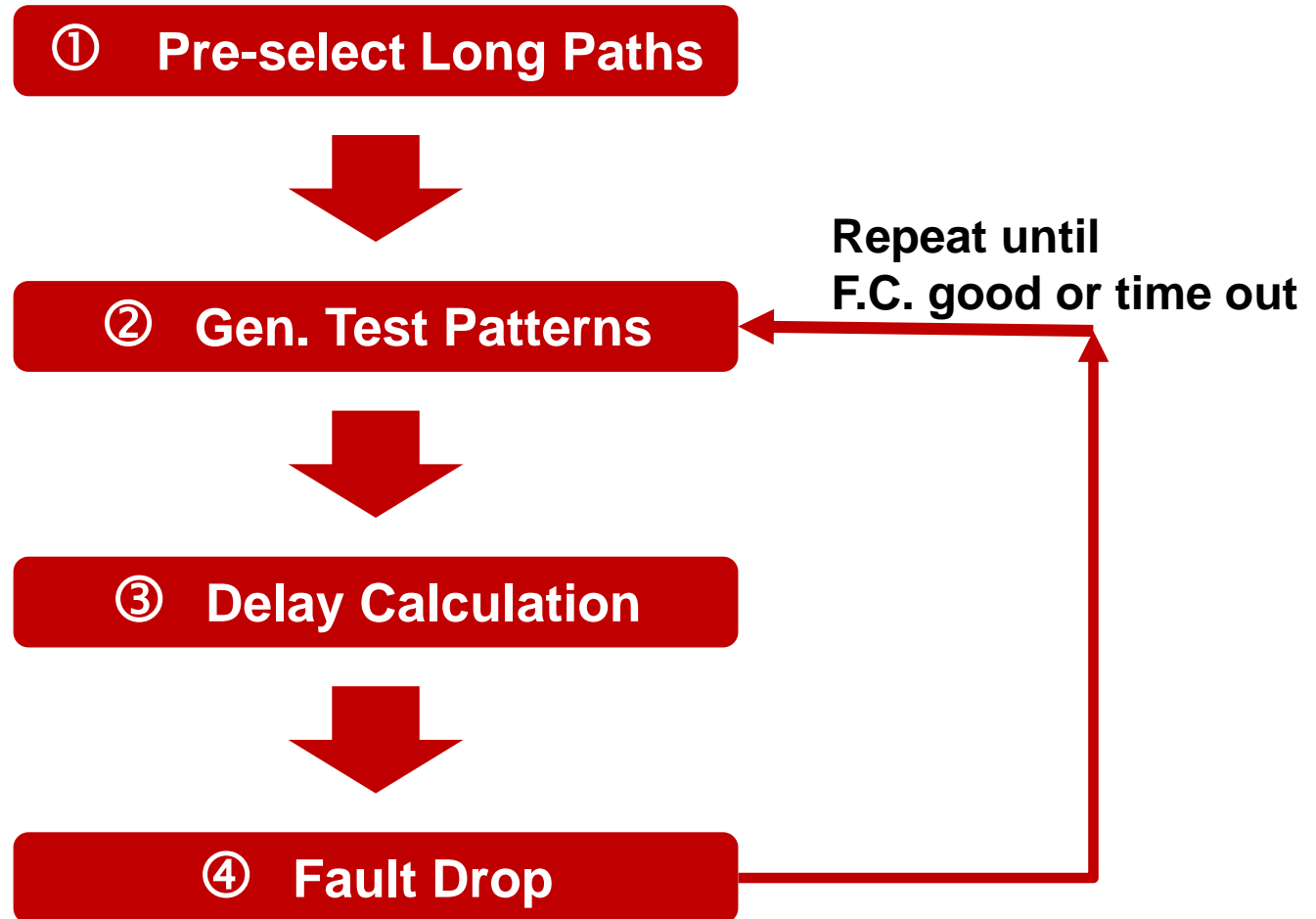


\* Lin's work use TDF  
(transition delay fault)


Other Ta-ATPG:  
ALAPTF [Gupta 04]  
KLPG [Qiu 04]  
Select long paths  
[Sharma 02][Ahmed 06]  
...
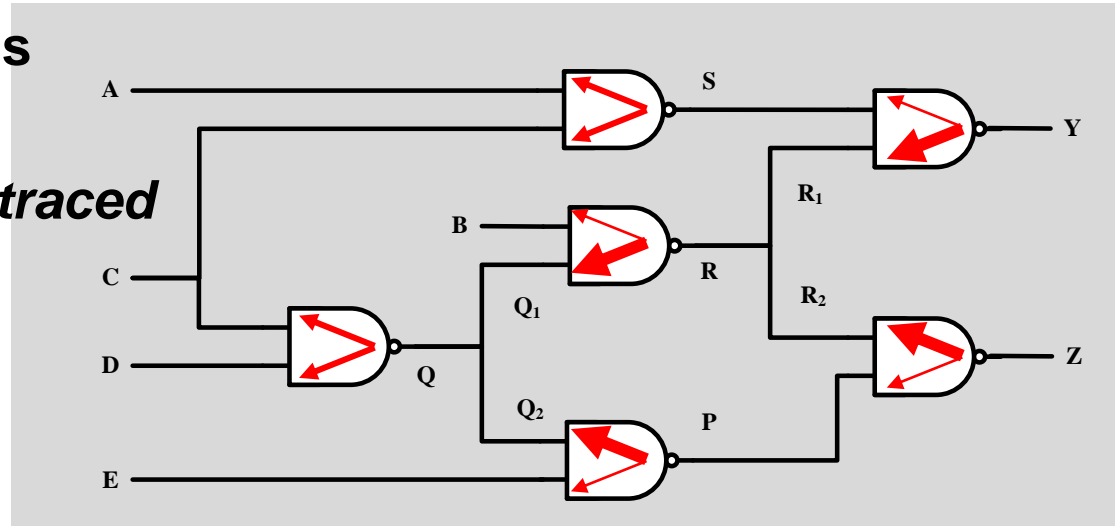
# ① Pre-select Act./Prop. Paths

- Pre-select **activation** paths
  - ♦ **Static** longer paths
  - ♦ More likely to be *backtraced*



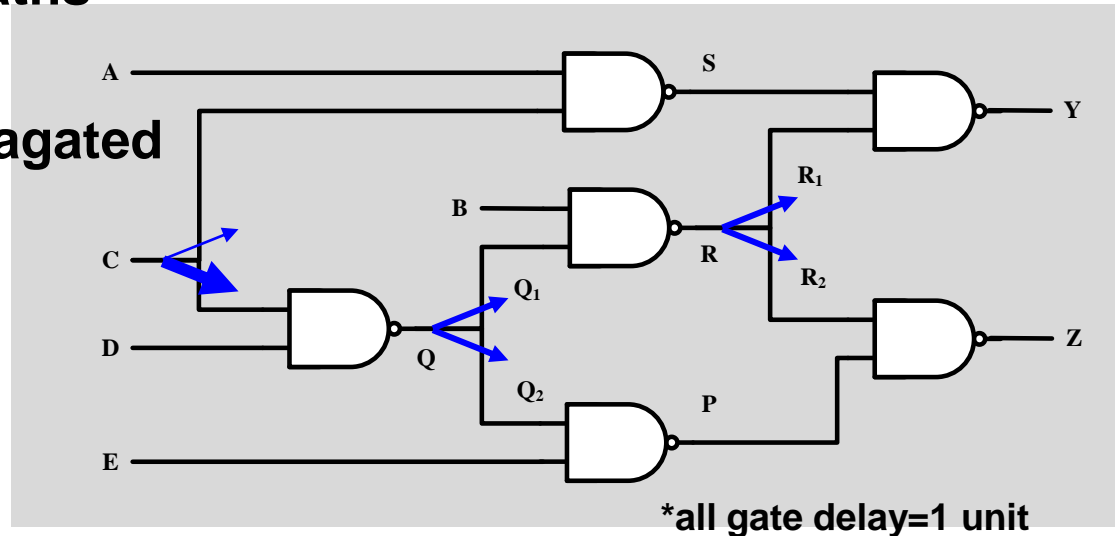- Pre-select **propagation** paths
  - ♦ **Static** longer paths
  - ♦ More likely to be propagated




- Static long paths
  - ♦ determined by STA


\*all gate delay=1 unit

## ② Generate Test Patterns

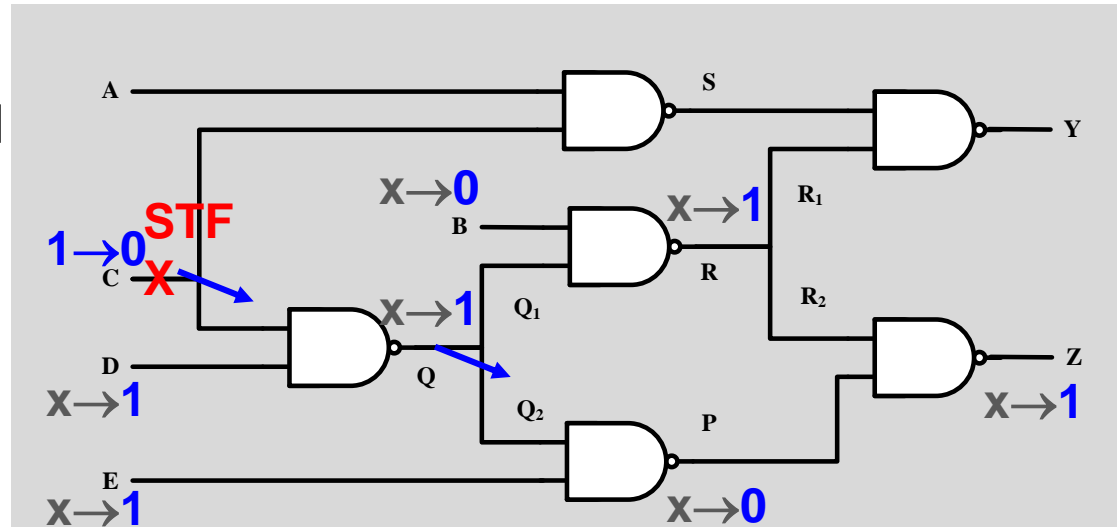- Example 1: **C STF**
  - ◆ Long path propagated



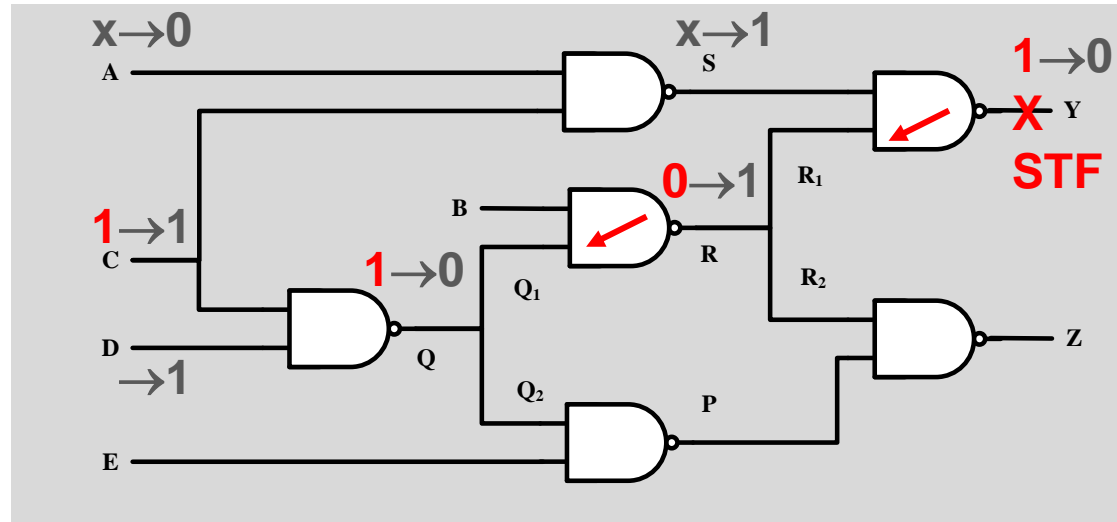- Example 2: **Y STF**
  - ◆ Long path activated






# Quiz

**Q:** Suppose inverter delay is 1 and the other gate delays are 2.  
Generate timing-aware test pattern for *H slow-to-rise* fault.

**A:**

	A	B	C	E	H	J	K
V1							
V2							

 

### ③ Delay Calculation, AT

- **Arrival Time**  $AT_x$  = time to **launch transition** from PI/PPI to node  $x$
- Calculate AT from input to output. Assign input transition  $AT_{PI} = 0$ 
  - ♦ If gate output  $x$  changes from controlled to non-controlled
 


$$AT_x = \max_{i \in I_{cn}} (AT_i + d_i)$$

$I_{nc}$  = gate inputs from controlling to non-controlling
  - ♦ If gate output  $x$  changes from non-controlled to controlled
 

$$AT_x = \min_{i \in I_{nc}} (AT_i + d_i)$$

$I_{nc}$  = gate inputs from non-controlling to controlling
  - ♦ If gate output  $x$  does not change
 

$AT_x = \text{N.A.}$

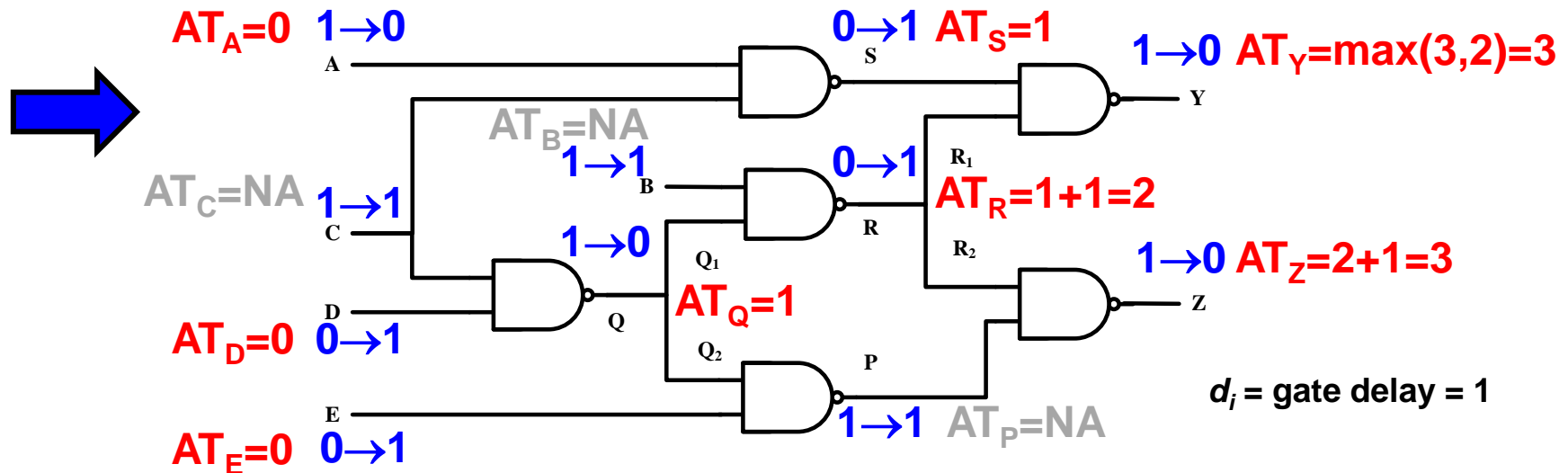

# How to Calculate PT?

- **Propagation time** ( $PT_x$ ) = time to propagate fault effect from  $x$  to PO/PPO
- Method 1: **Forward** calculation fault by fault

- ♦ Slow, overlapped calculation

- ♦ Example:

- \*  $R \rightarrow Y, R \rightarrow Z$
- \*  $Q \rightarrow Y, Q \rightarrow Z$
- \*  $D \rightarrow Y, D \rightarrow Z$

- Method 2: **Non-robust** path **backtrace**



- ♦ **Side input is non-controlling at  $V_2$**

- \* (See Video 9.2)

- ♦ Fast, no calculation overlap

- ♦ Example:

  - \*  $YZ \rightarrow SRP \rightarrow QA \rightarrow CD$
- \* E and B Not traced



**Method 2 (Backward) is Better**

### ③ Delay Calculation, PT



- Calculate PT from output to input, trace **non-robust sensitized** paths

$$PT_i = \begin{cases} PT_o + d_i, & \text{if gate is NR sensitized} \\ NA, & \text{if gate is not NR sensitized} \end{cases}$$

- PT of fan out stem = maximum of PT of its branches\*

$$PT_{stem} = \max_{i \in branches} (PT_i)$$

 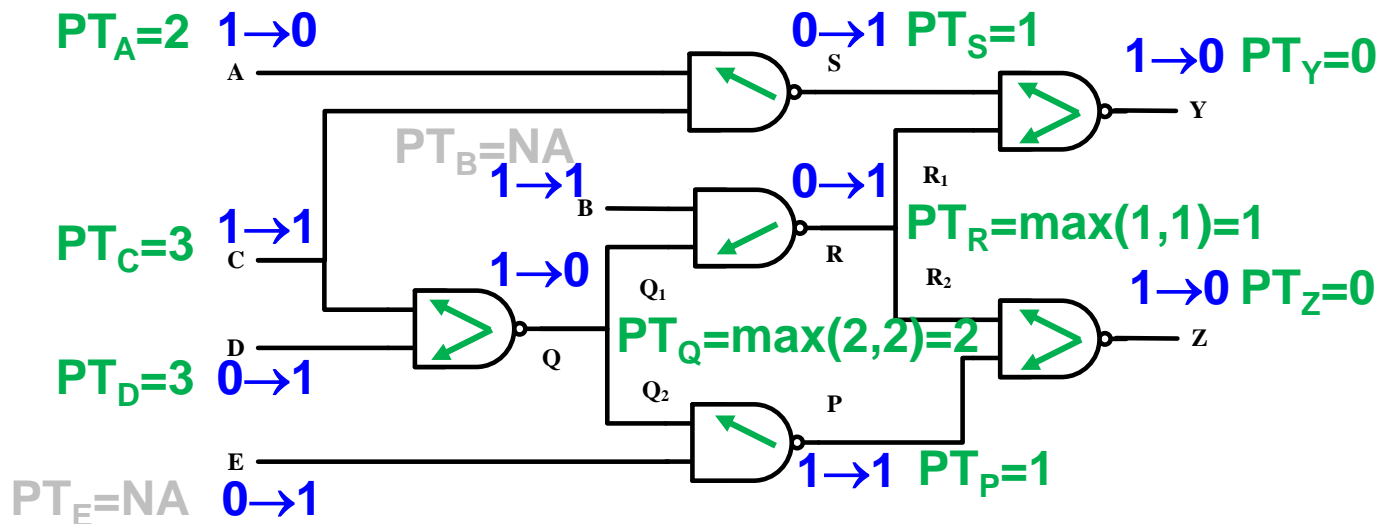*\*Reconverged fanout branches must be handled carefully*




### ③ Delay Calculation, PD

- Propagation Delay**  $PD_x$  = time to travel from PI/PPI to PO/PPO through  $x$


$$PD_x = AT_x + PT_x$$

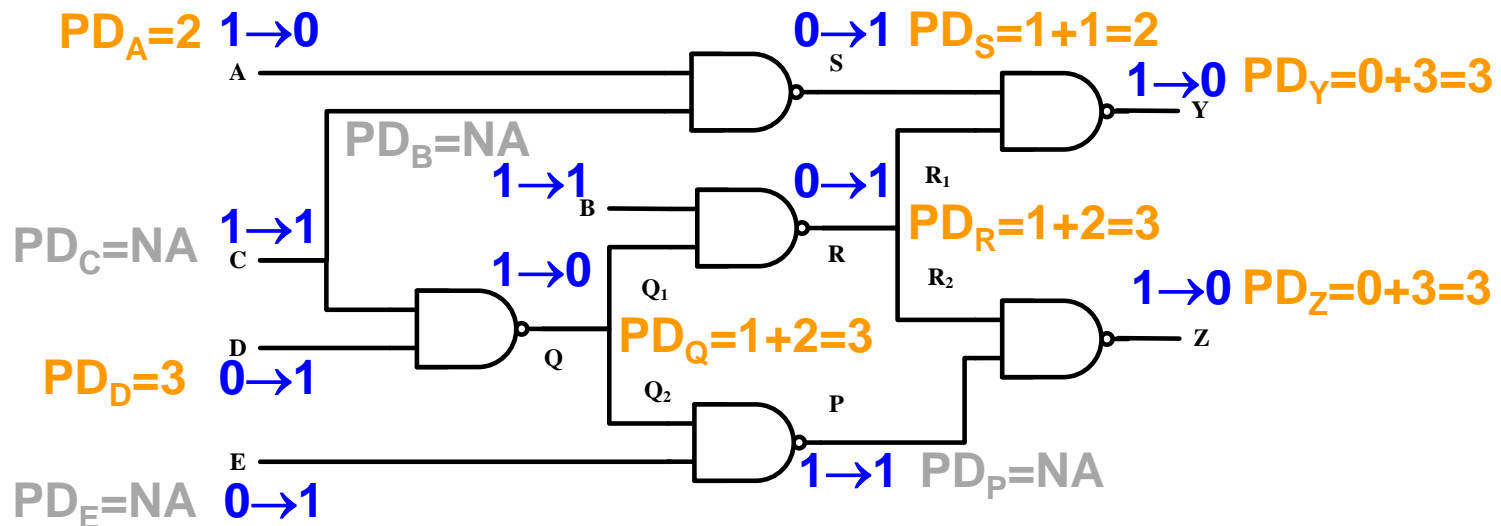- $PD_x = NA$  if  $PT_x = NA$  or  $AT_x = NA$ 
  - ♦  $C$  and  $P$  are  $NA$  because  $AT = NA$
  - ♦  $E$  and  $B$  are  $NA$  because  $PT = NA$


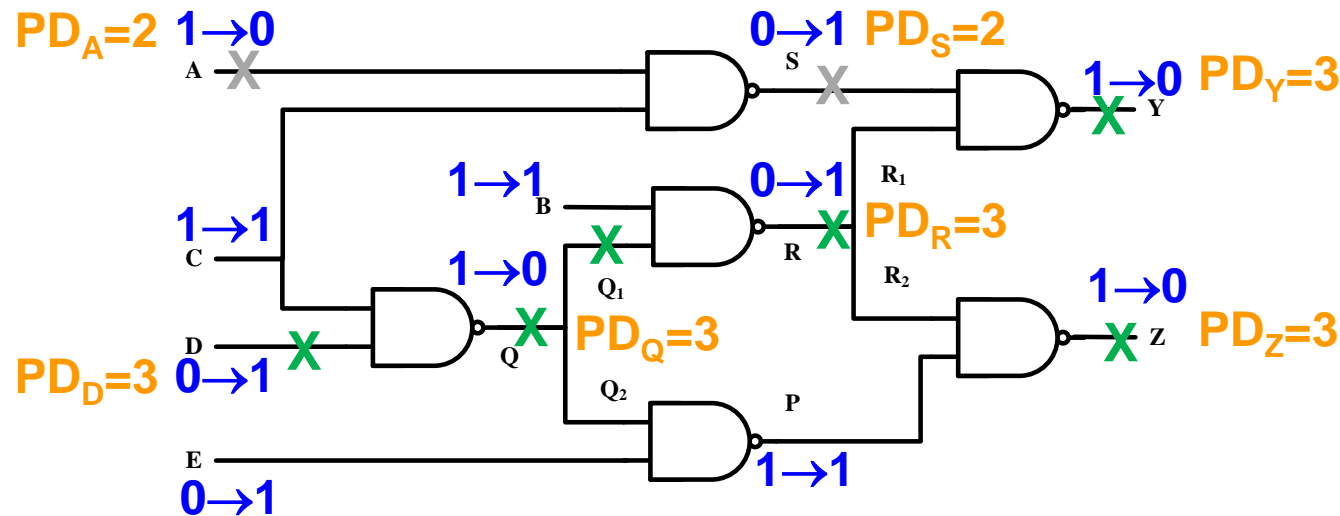
## ④ Fault Drop

- Fault  $f$  is **dropped** when two conditions met
  - 1) **TDF  $f$  is detected**:  $AT \neq NA$  and  $PT \neq NA$  (WHY? FFT)
  - 2)  **$PD_f$  is long enough\*** \*user defined fault drop criteria
- Example: assume  **$PD_f \geq 3$**  to be dropped
  - 1) 8 TDF faults detected
  - 2) but **only 6 of them** can be dropped




$$Fault\ Coverage_{TA} = \frac{\text{number of dropped TDF}}{\text{number of total TDF}} \times 100\%$$

# Quiz

Q1: Suppose inverter delay is **1** and the other gate delays are **2**.  
What is  $PD_E$ ?


Q2: Suppose fault drop criterion is  $PD > 4$ . Can we drop **E STF** fault?

	A	B	C	E	H	J	K
AT							
PT							
PD							

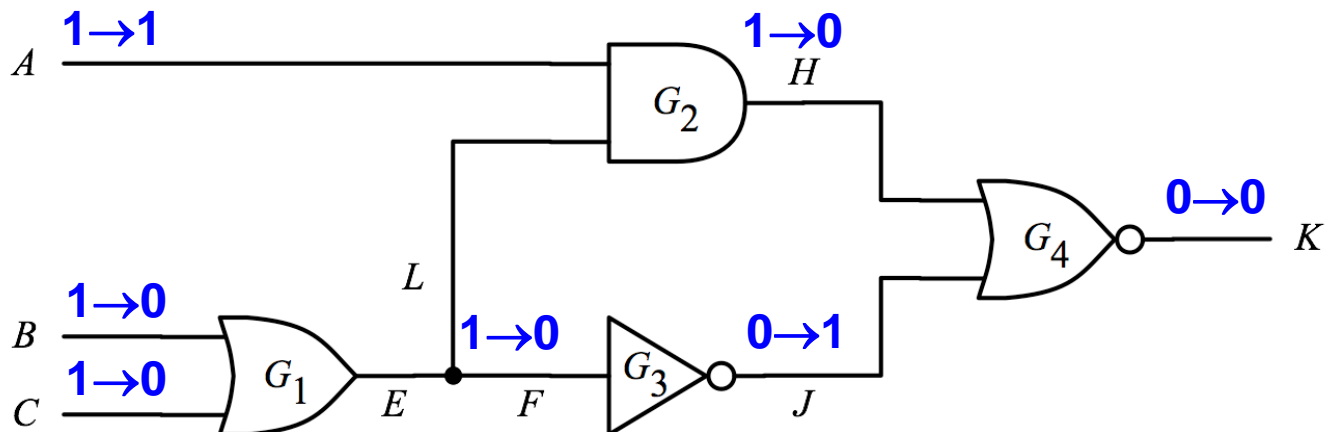
 
# LSI Logic Experiment [Turakhia 07]

- Total **32K** chips tested, **23** small delay defects
  - ♦ Before stress : **1** escaped slow test but fail fast functional test (31 DPM)
  - ♦ After stress, **4** failed (124 DPM), **18** passed (557 DPM)






# Summary

- **Small delay defects (SDD)** important for modern technologies
  - ◆ How to detect? **Faster test** or longer sensitization paths
- **Timing-aware ATPG** tries to
  - ◆ **Activate** long paths or **Propagate** fault effect through long paths
- **Algorithm example**
  - ① Pre-select long paths
  - ② Generate test patterns
  - ③ Calculate **AT, PT, PD**
  - ④ Drop faults that meet criteria
- **Advantage of Ta-ATPG**
  - ◆ 😊 Detect SDD : reduce DPM or potential reliability issues
- **Disadvantages of Ta-ATPG**
  - ◆ 😞 Longer test length   😞 Run time overhead

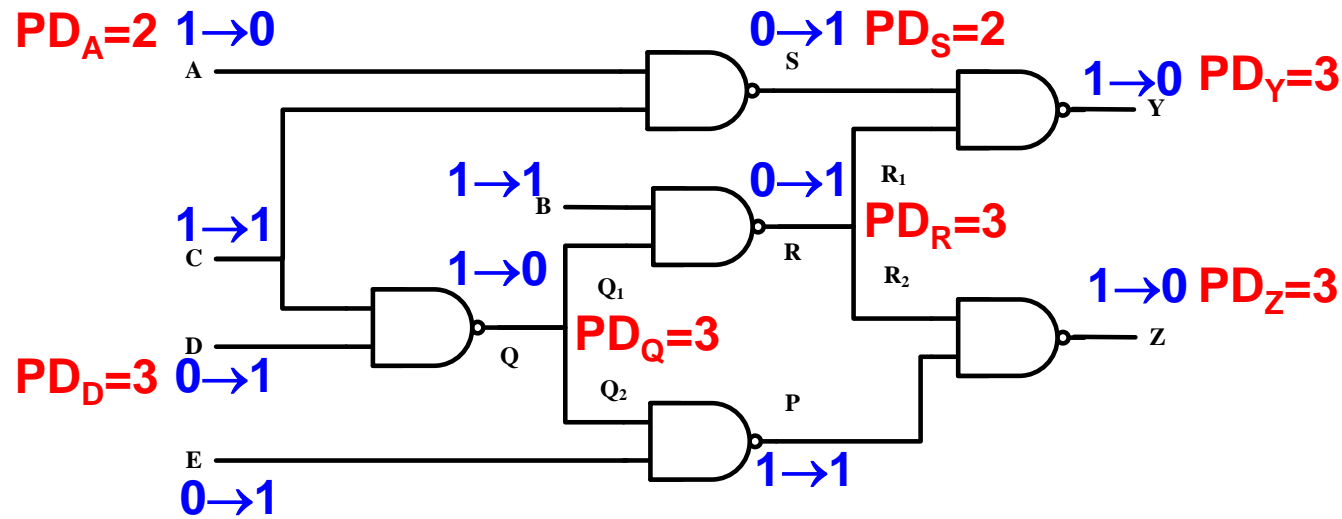
# FFT

- Q: A STF is NOT dropped because  $PD_f < 3$ 
  - ♦ How can we drop A STF?



# FFT

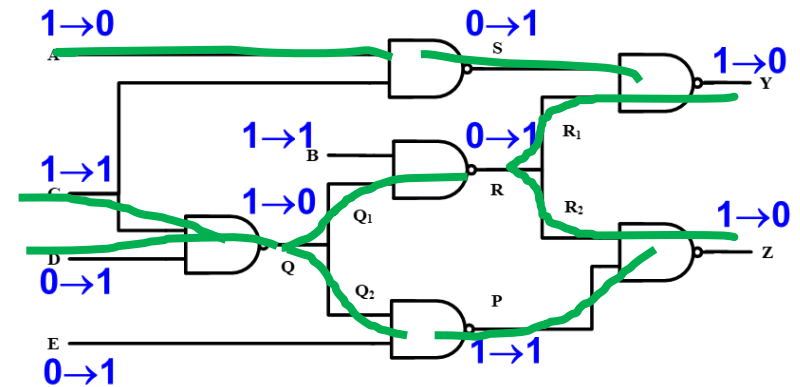- Q1: TDF  $f$  is **detected** (i.e.  $AT \neq NA$  and  $PT \neq NA$ ). Why?
- Q2: Any exception where fault  $f$  is detected but  $AT=NA$  or  $PT=NA$  ?



# References

- [Ahmed 06] N. Ahmed, M. Tehranipoor and V. Jayaram, "Timing-based delay test for screening small delay defects," 2006 43rd ACM/IEEE Design Automation Conference, 2006, pp. 320-325.
- [Gupta 04] P. Gupta and M. S. Hsiao, "ALAPTF: a new transition fault model and the ATPG algorithm," 2004 International Conference on Test, 2004, pp. 1053-1060.
- [Lin 06] X. Lin et al., "Timing-Aware ATPG for High Quality At-speed Testing of Small Delay Defects," 2006 15th Asian Test Symposium, 2006, pp. 139-146.
- [Qiu 04] W. Qiu et al., "K longest paths per gate (KLPG) test generation for scan-based sequential circuits," 2004 International Conference on Test, 2004, pp. 223-231.
- [Sato 05] Y. Sato, S. Hamada, T. Maeda, A. Takatori and S. Kajihara, "Evaluation of the statistical delay quality model," Proceedings of the ASP-DAC 2005. Asia and South Pacific Design Automation Conference, 2005.
- [Sharma 02] M. Sharma and J. H. Patel, "Finding a small set of longest testable paths that cover every gate," Proceedings. International Test Conference, 2002, pp. 974-982.
- [Tseng 01] C.W. Tseng , " Multiple-output propagation transition fault test," Int'l Test Conf., 2001.
- [Turakhia 07] R. Turakhia, W. R. Daasch, M. Ward and J. Van Slyke, "Silicon evaluation of longest path avoidance testing for small delay defects," 2007 IEEE International Test Conference, 2007, pp. 1-10,