

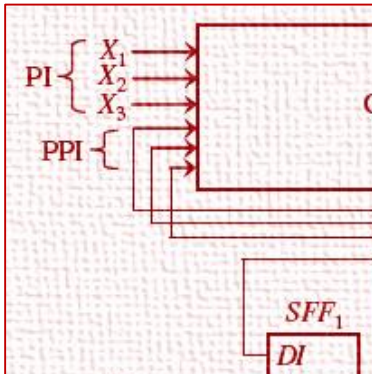
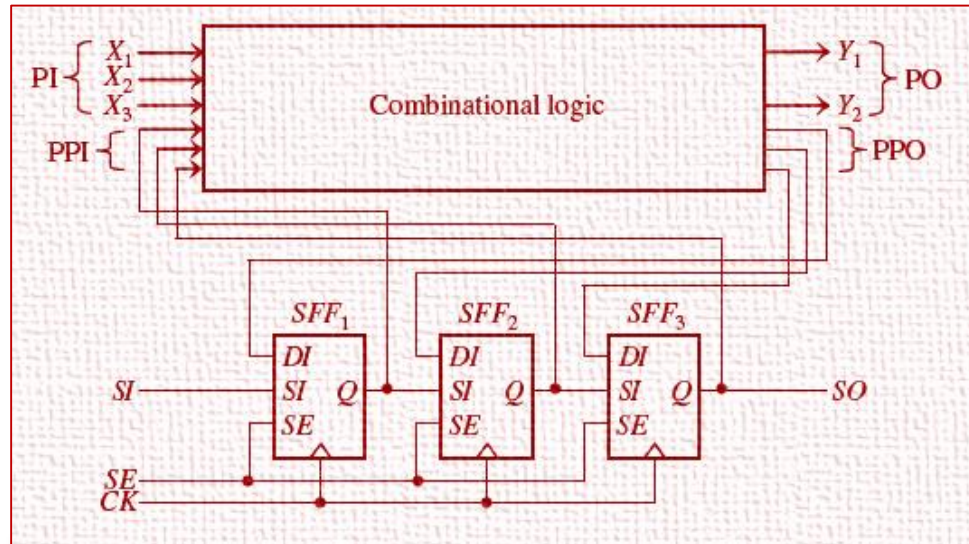
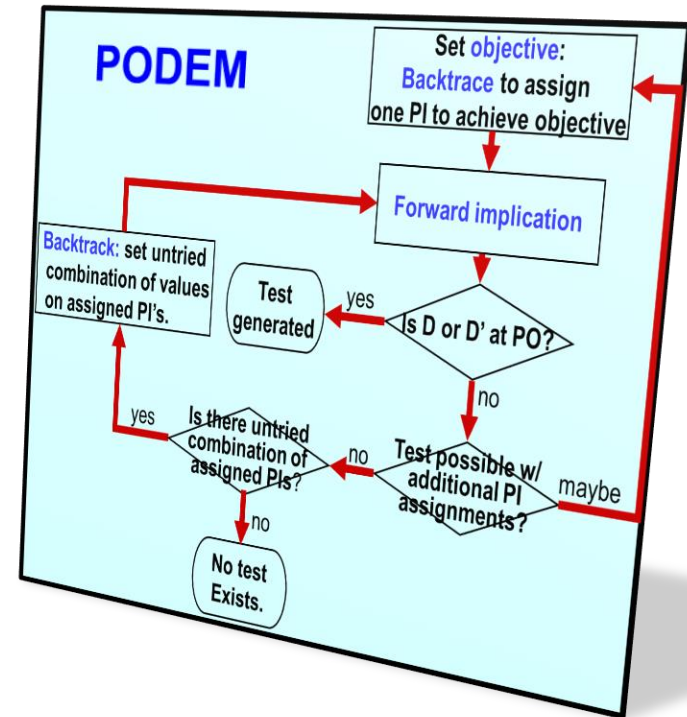


DFT - Part 1

- Introduction
 - Internal Scan
 - ◆ FF-based
 - * MUXed-D scan (1973, Stanford)
 - MUXed-D scan flip-flop
 - Test Mode Operation
 - Ckt. Model for ATPG
 - ◇ SSF
 - ◇ LOS
 - ◇ LOC
 - * Clocked scan
 - * Other scan
 - ◆ Latch-based
- 
- The diagram illustrates a MUXed-D scan flip-flop circuit. It features a main block with multiple inputs on the left. The top three inputs are grouped under the label 'PI' and are labeled X_1 , X_2 , and X_3 . Below these are two inputs grouped under the label 'PPI'. The circuit also includes a clock input (indicated by a triangle symbol) and a 'DI' (Data Input) input. The output of the flip-flop is labeled 'Q'. A sub-block labeled 'SFF₁' is shown at the bottom right, with its own 'DI' input.


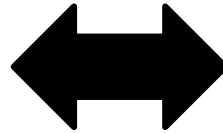


How to Run Comb. ATPG on Seq. Ckt?

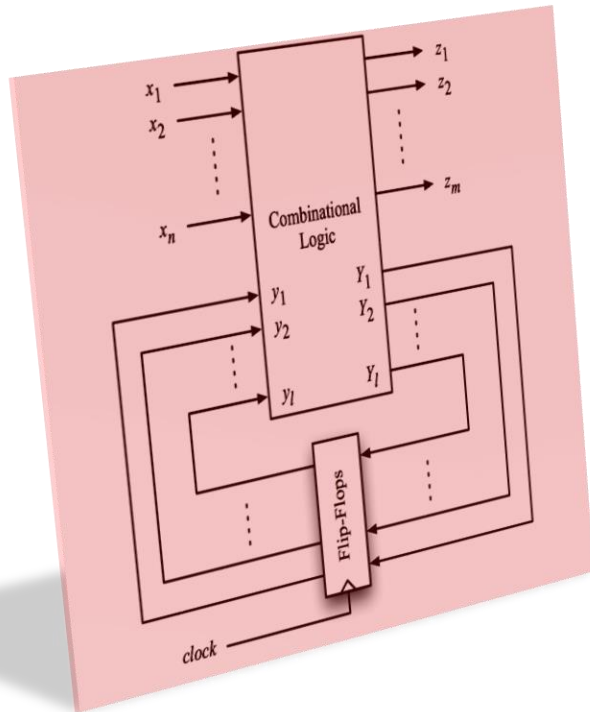

DFT Turns Seq. Ckt. to Comb. Ckt.

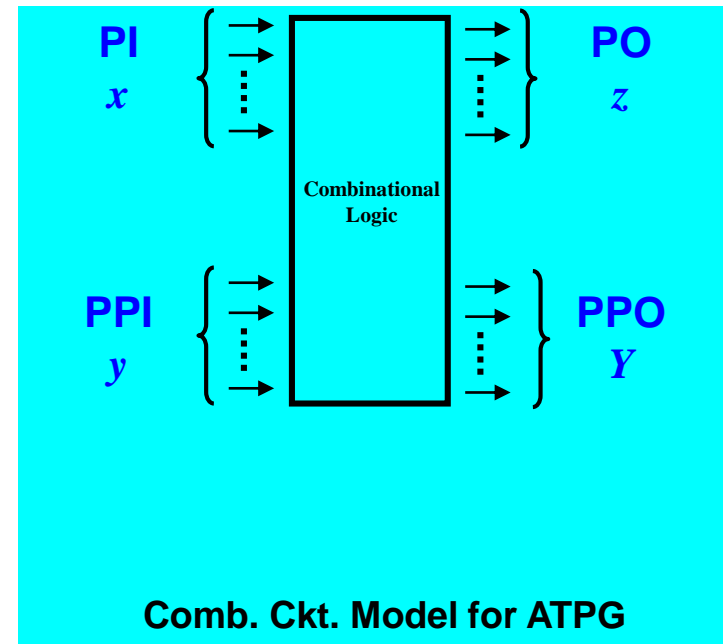
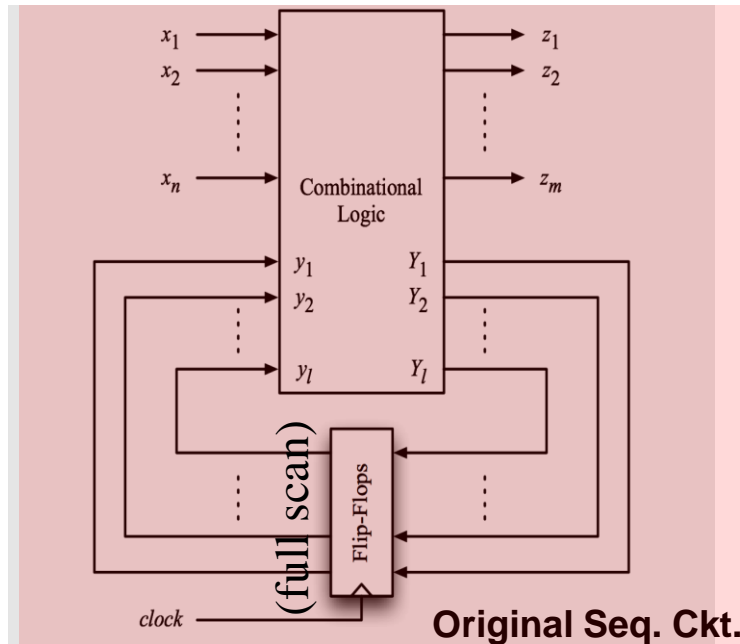
- DFT turns sequential ckt into combinational ckt in test mode
 - ♦ ATPG sees only **comb. ckt. model**
- Scan FF become **Pseudo Primary Input (PPI)**, fully controllable
- Scan FF become **Pseudo Primary Output (PPO)**, fully observable



Comb. ATPG Much Faster than Seq. ATPG

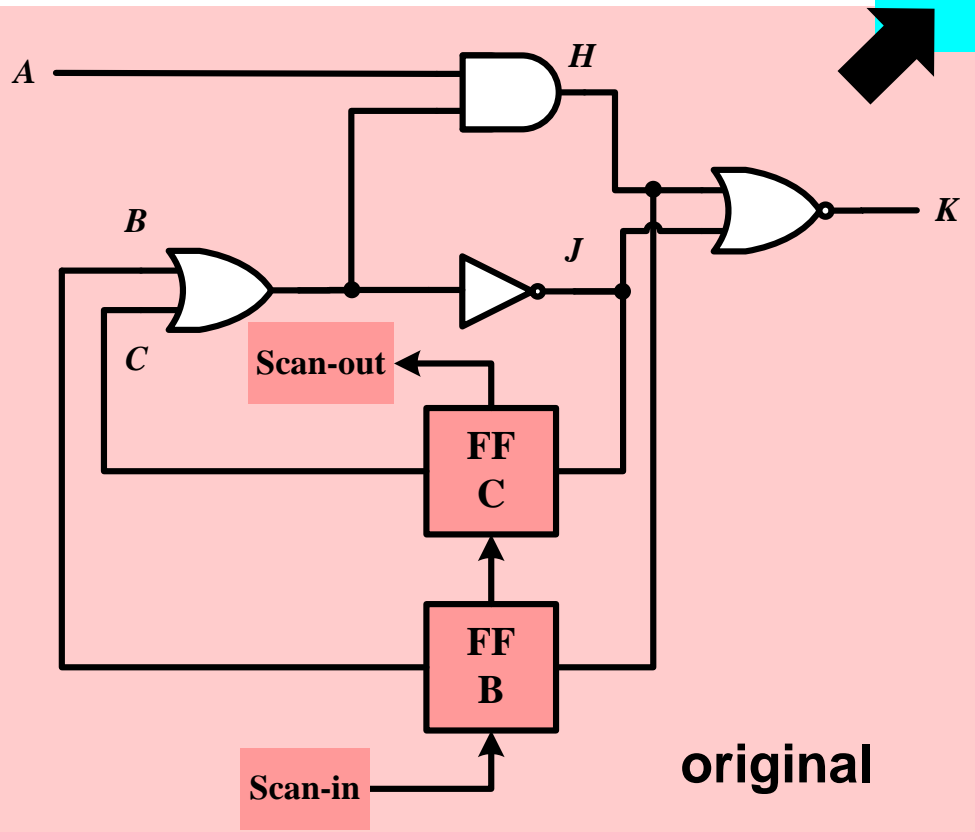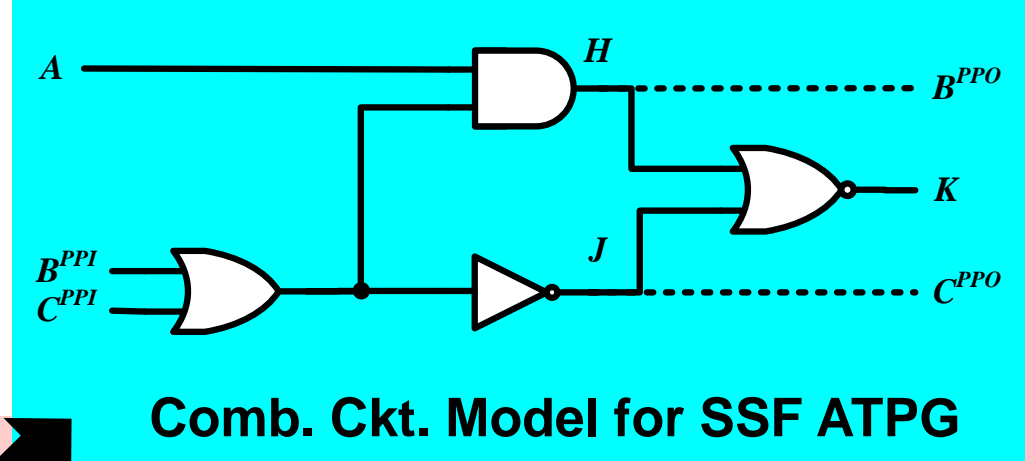Example (1/2)

- Two scan FF in a scan chain
- SI → FF-B → FF-C → SO




- A is **PI**
- B,C are **PPI**
- K is **PO**
- HJ are **PPO**
 - ◆ $H=B^{PPO}, J=C^{PPO}$

**NOTE: this model assume
no fault in FF. (see FFT)**

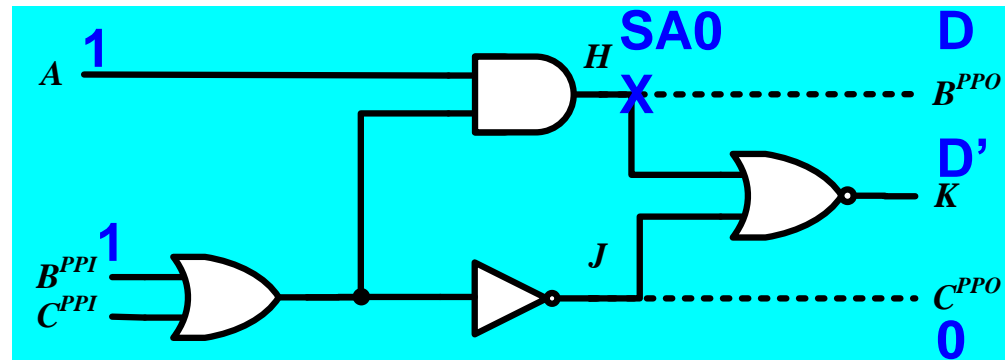
Example (2/2)

- Generate SSF ATPG pattern
 - ◆ H SA0 fault



| PI | PPI | PO | PPO |
|----|------------------|------|------------------|
| A | $B^{PPI}C^{PPI}$ | K | $B^{PPO}C^{PPO}$ |
| 1 | 1 X | D' | D 0 |

comb. pattern

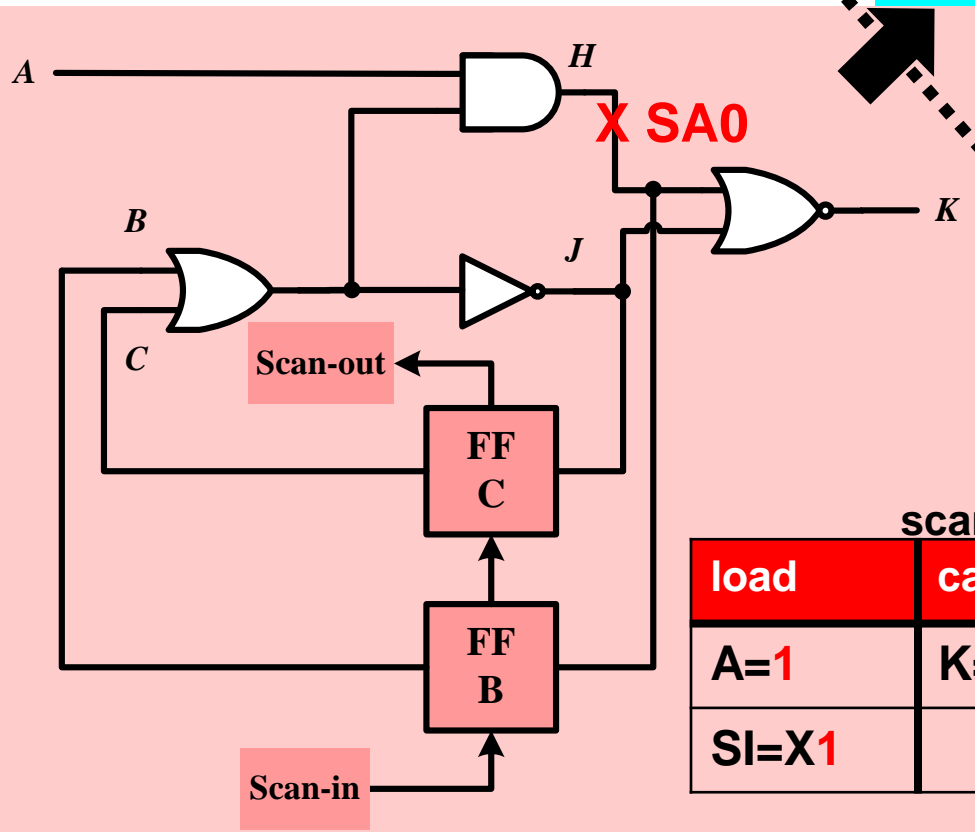

scan pattern


| load | capture | unload |
|-------|---------|--------|
| A=1 | K=L | |
| SI=X1 | | SO=LH |

Quiz

Q1: Convert seq. ckt. into comb. ckt. model for SSF ATPG.

Q2: Generate a test pattern for SA1 fault.


(show comb. pattern)

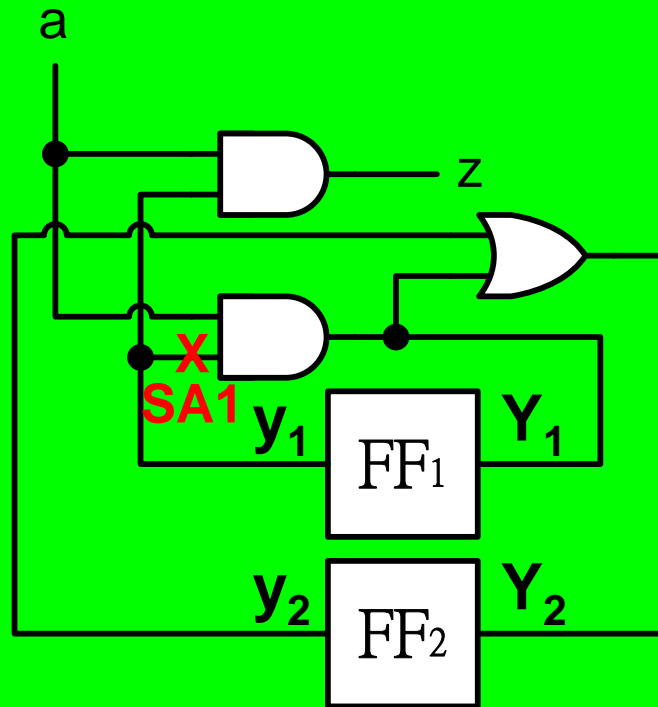

| PI | PPI | PO | PPO |
|----|-------------------------------|----|-------------------------------|
| a | y ₁ y ₂ | z | Y ₁ Y ₂ |
| | | | |

DFT - Part 1




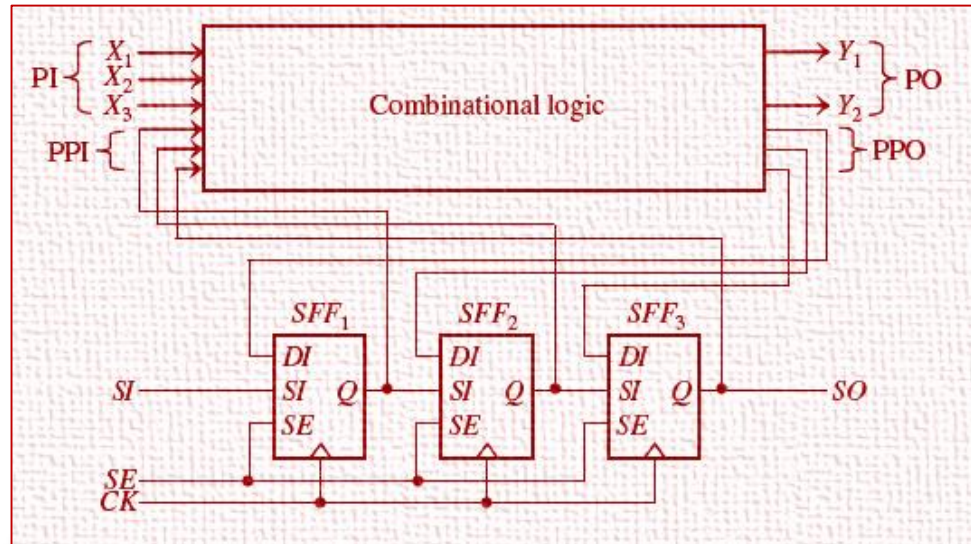
- Introduction
- Internal Scan
 - ◆ FF-based
 - * MUXed-D scan (1973, Stanford)
 - MUXed-D scan flip-flop
 - Test Mode Operation
 - Ckt Model for ATPG
 - ◇ SSF
 - ◇ LOS
 - ◇ LOC
 - * Clocked scan
 - * Other scan
 - ◆ Latch-based



Model for LOS ATPG

- LOS for Transition Delay Fault

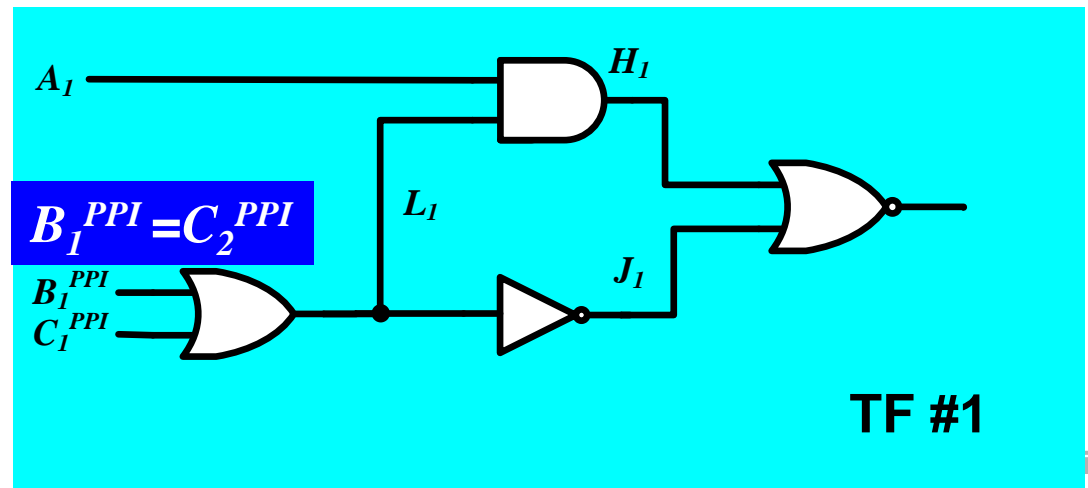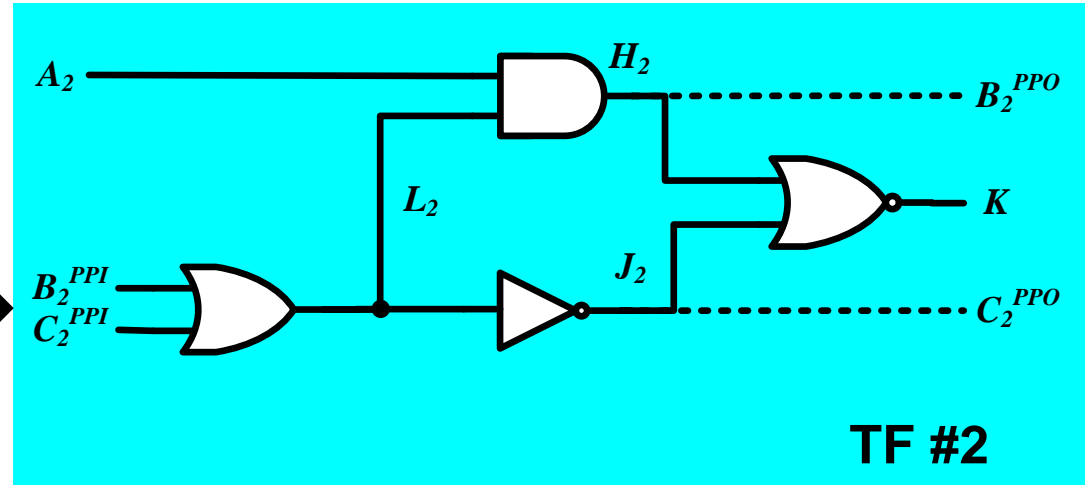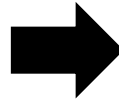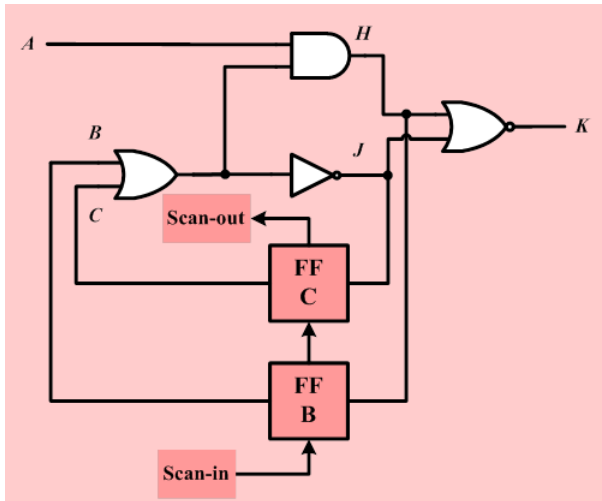- ♦ 1. Generate SSF pattern V_2 in time frame TF#2
- ♦ 2. Then apply constraints to generate V_1 in time frame TF#1




Subscripts = time frame
Why TF#2 first? see FFT

LOS Example (1/2)

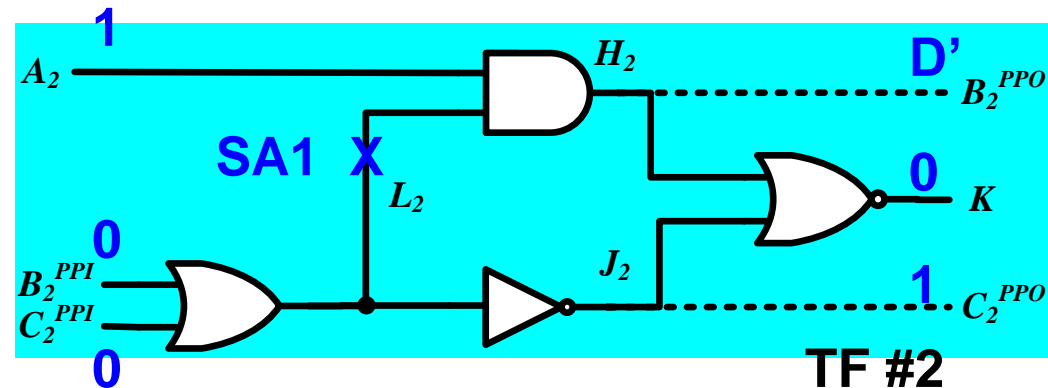- Example: *L* slow-to-fall (STF) fault


Time frame #2:

- Inject *L*₂ SA1
- $B_2^{PPI}=0$, $C_2^{PPI}=0$, $A_2^{PI}=1$
- $B_2^{PPO} = D'$





Time frame #1:

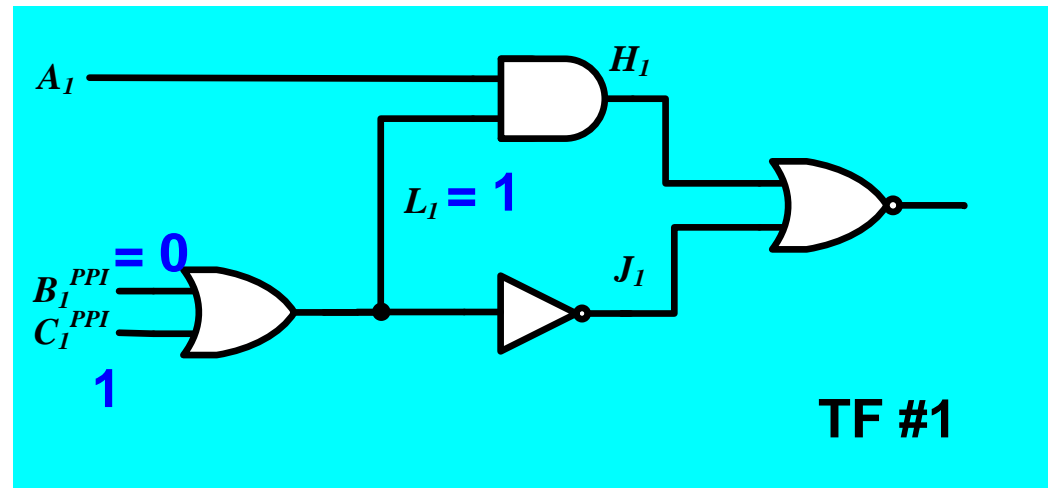- STF fault constraint: $L_1 = 1$
- LoS constraint: $B_1^{PPI}=C_2^{PPI}=0$
- so, $C_1^{PPI}=1$



Only One Time Frame Memory Needed

LOS Example (2/2)

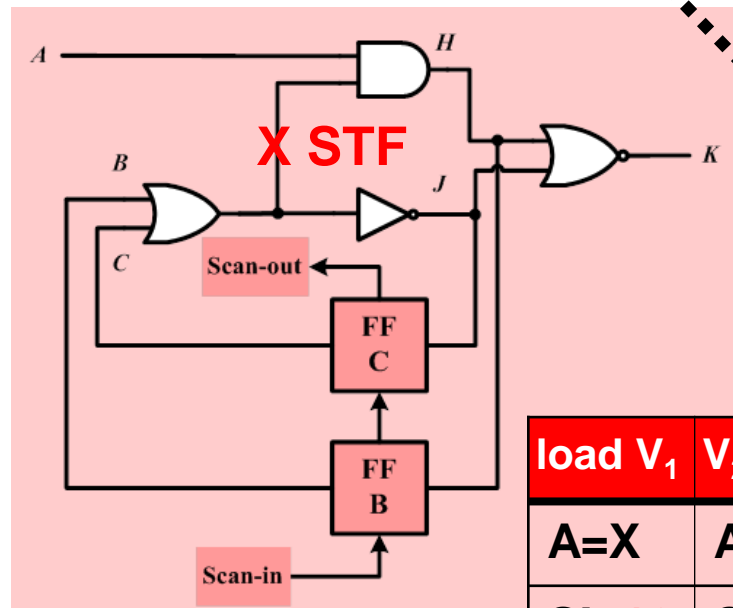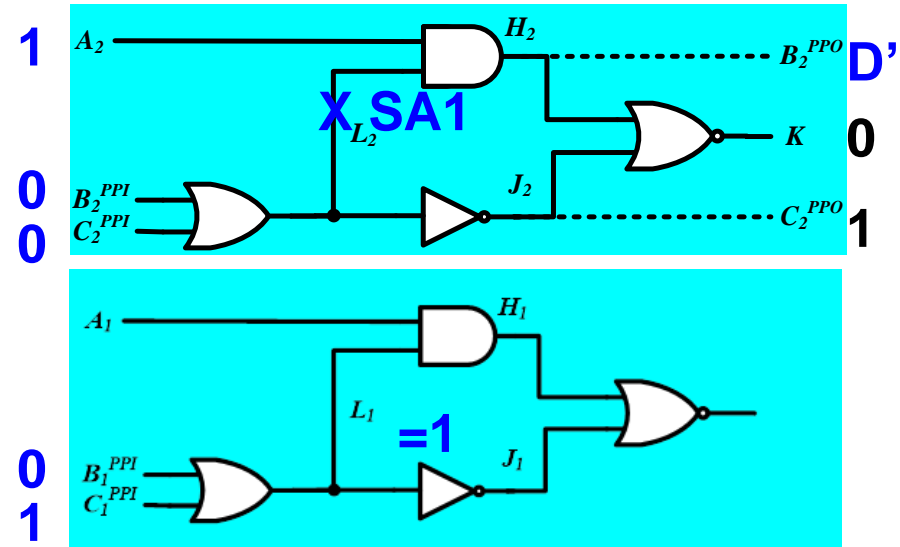

| V_1 | | V_2 | | PO | PPO |
|-------|-------------|-------------|---|-------------|-------------|
| A | B_1^{PPI} | C_1^{PPI} | A | B_2^{PPI} | C_2^{PPI} |
| X | 0 | 1 | 1 | 0 | 0 |
| | | | | K | B_2^{PPO} |
| | | | | | C_2^{PPO} |


| load | V_1 | V_2 | capture | unload |
|-------|-------|-------|---------|--------|
| A=X | | A=1 | K=L | |
| SI=10 | | SI=0 | | SO=HL |

Quiz

Q: Generate LOS test pattern for STF fault.


suppose $SI \rightarrow FF_2 \rightarrow FF_1 \rightarrow SO$

(show comb. pattern)

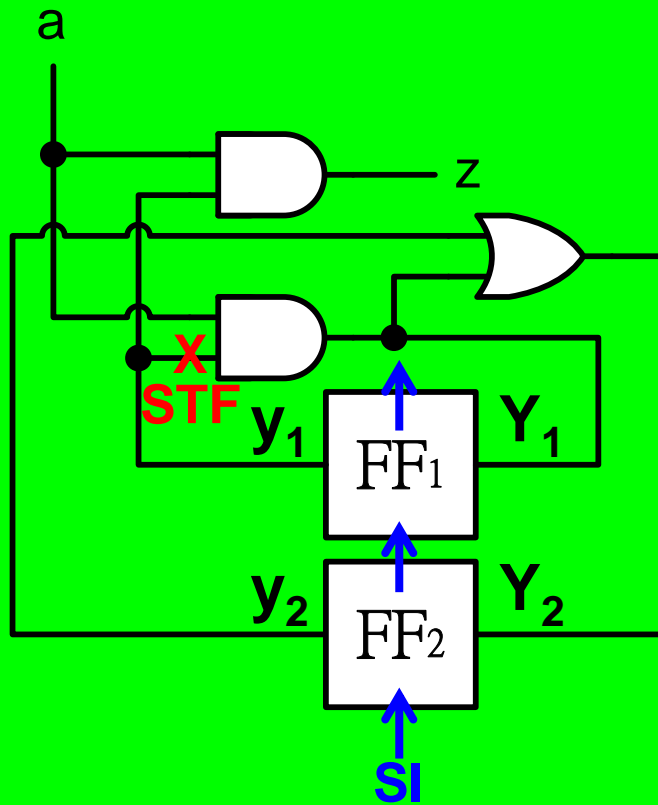

DFT - Part 1

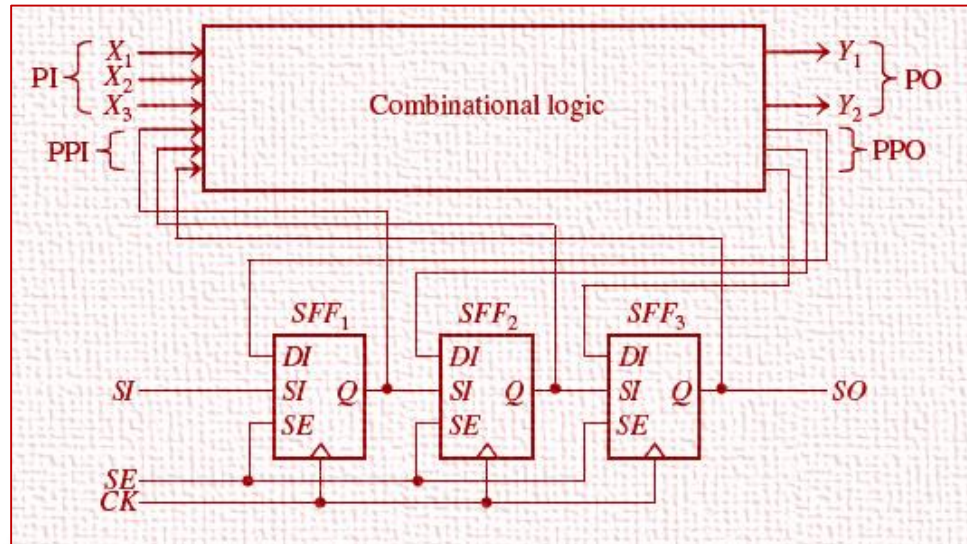- Introduction
- Internal Scan
 - ◆ FF-based
 - * MUXed-D scan (1973, Stanford)
 - MUXed-D scan flip-flop
 - Test Mode Operation
 - Ckt Model for ATPG
 - ◇ SSF
 - ◇ LOS
 - ◇ LOC
 - * Clocked scan
 - * Other scan
 - ◆ Latch-based




LOS Untestable

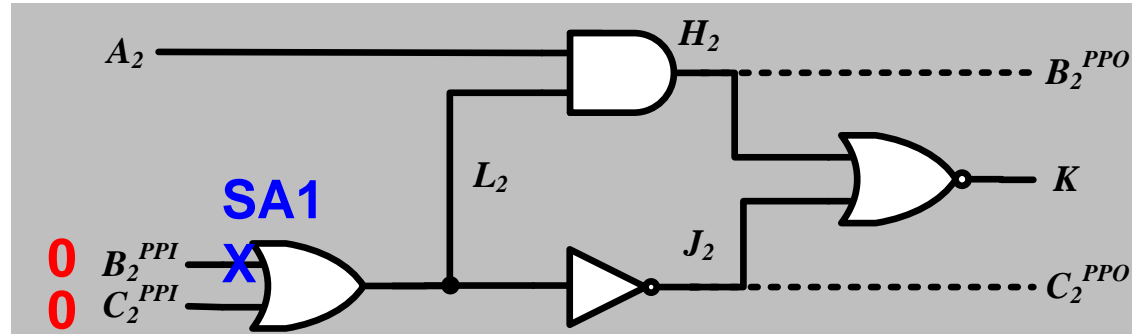- **Example: *B* slow-to-fall (STF) fault**


Time frame #2:

- Inject B_2^{PPI} SA1
- $B_2^{PPI}=0$, $C_2^{PPI}=0$
- $C_2^{PPO} = D$



Time frame #1:

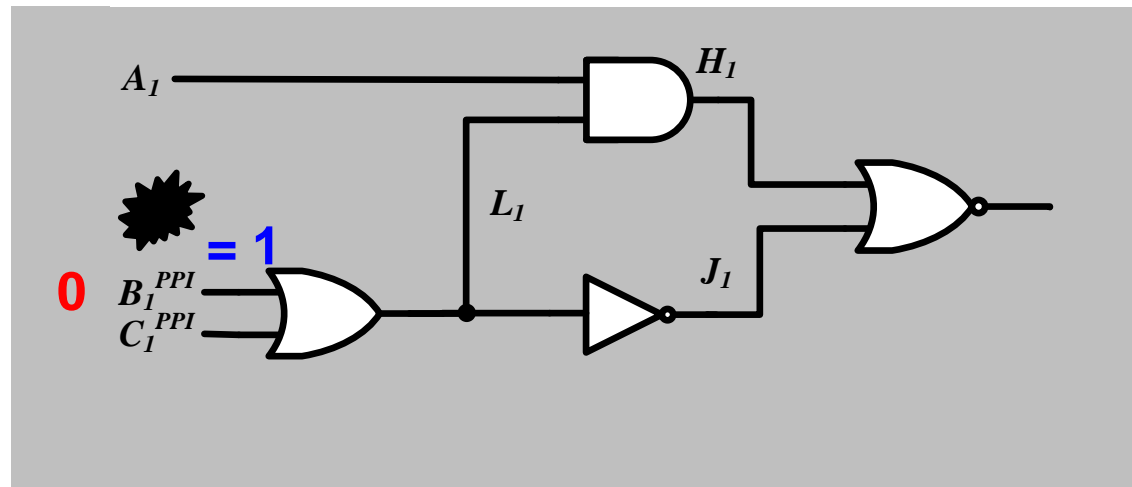- **Fault constraint:** $B_1^{PPI} = 1$
- **LoS constraint:** $B_1^{PPI} = 0$
- **Conflict!**





LOS Untestable due to Structural Dependency

Model for LOC ATPG

- LOC for TDF ATPG


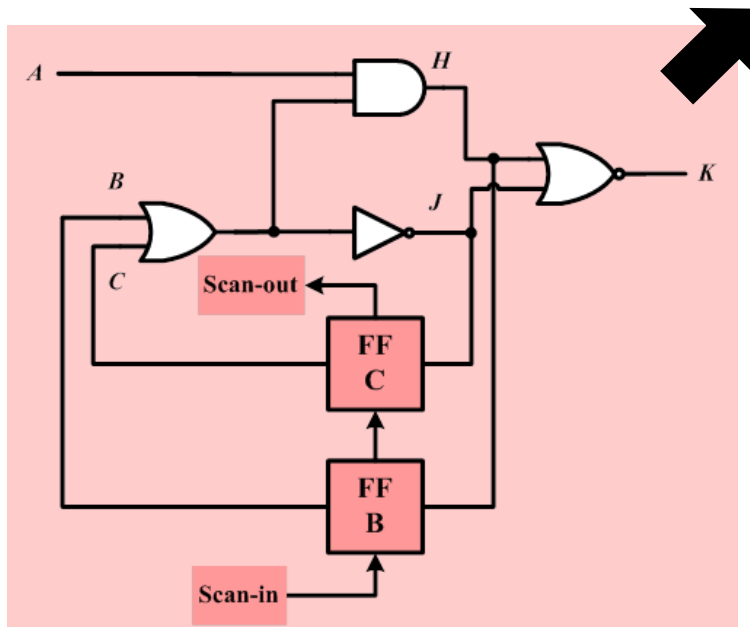
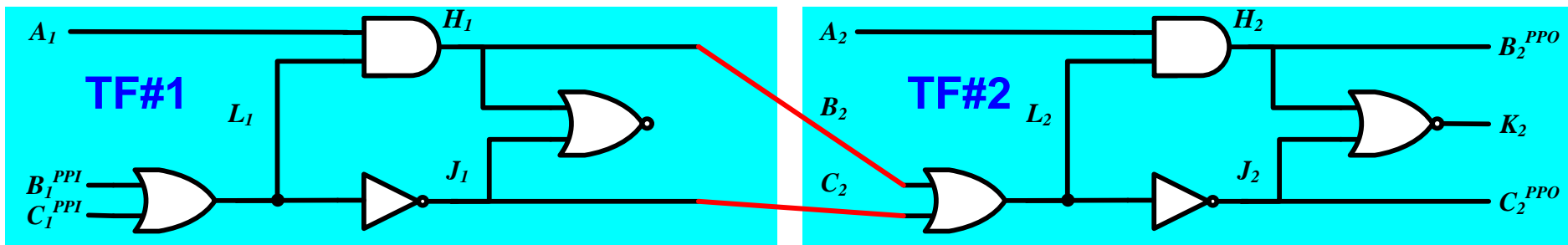
- ◆ 1. Duplicate combinational Ckt into two copies: **TF#1** and **TF#2**
- ◆ 2. Connect TF#1 and TF#2 as one big ckt



**LOC Needs
Time Frame Expansion**

LOC Example (1/2)

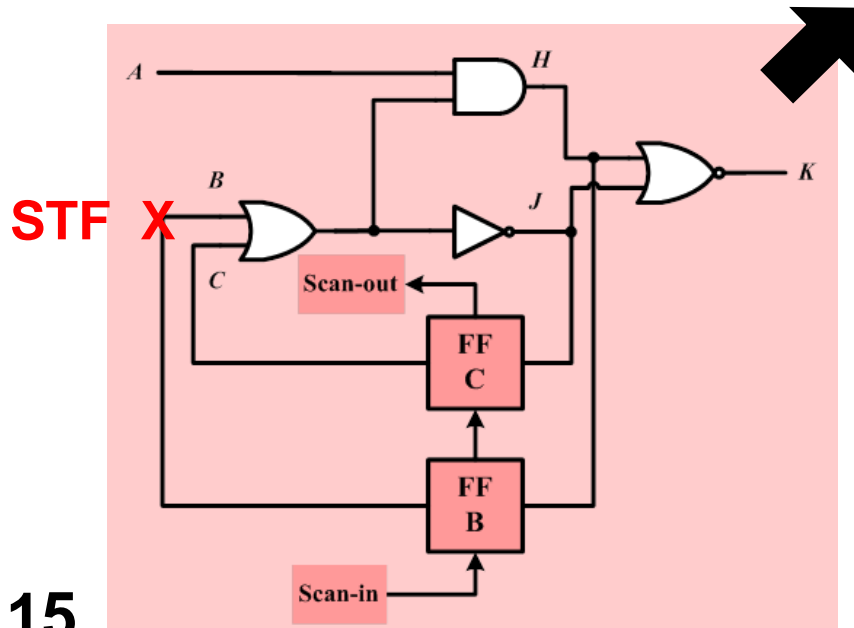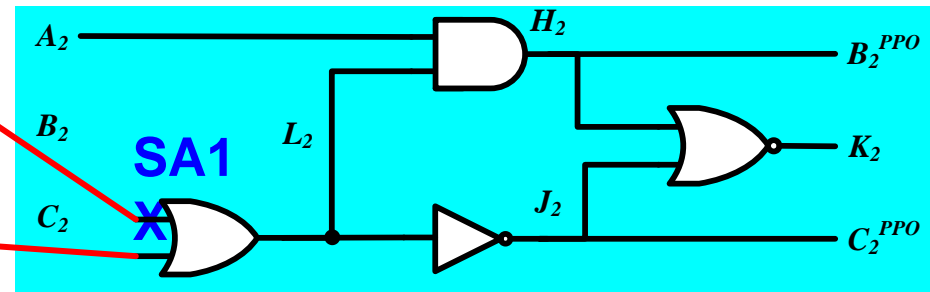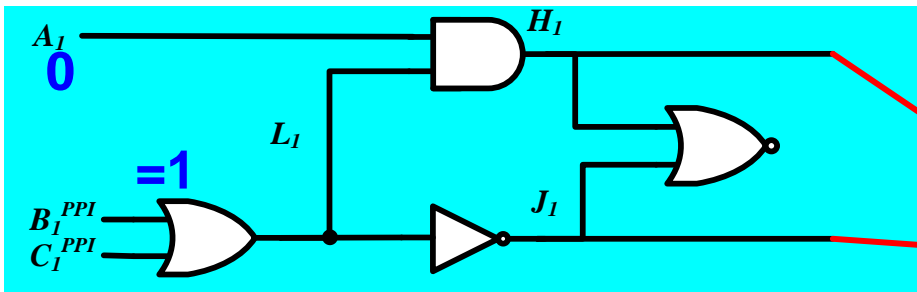
- Example: *B slow-to-fall (STF)* fault
 - ♦ SSF ATPG B_2 SA 1 fault
 - ♦ with constraint $B_1^{PPI}=1$




- PODEM
- Objective: $B_2=0$
 - ♦ Backtrace $A_1=0$
- Objective: $C_2=0$
 - ♦ Backtrace $B_1^{PPI}=1$
- Simulate $C_2^{PPO} = D$

Now It is LOC Testable!

LOC Example (2/2)

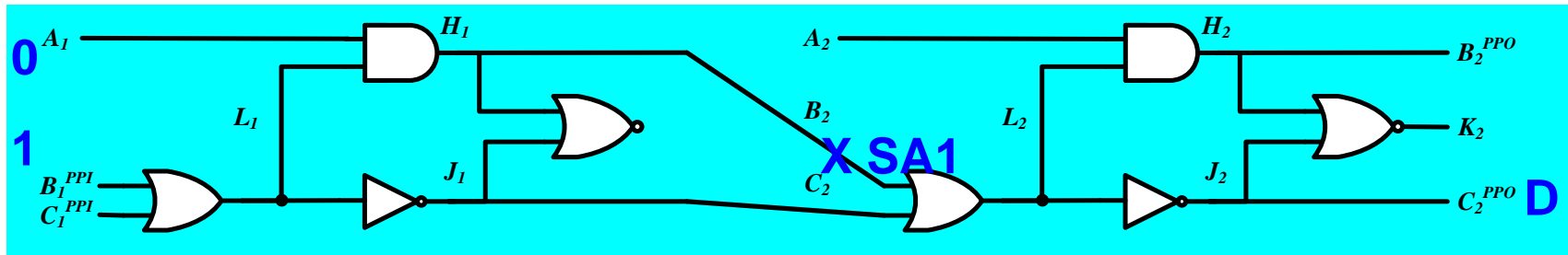

| V ₁ | | V ₂ | PO | PPO |
|----------------|---|----------------|----|---|
| A ₁ | B ₁ ^{PPI} C ₁ ^{PPI} | A ₂ | K | B ₂ ^{PPO} C ₂ ^{PPO} |
| 0 | 1 X | X | X | X D |

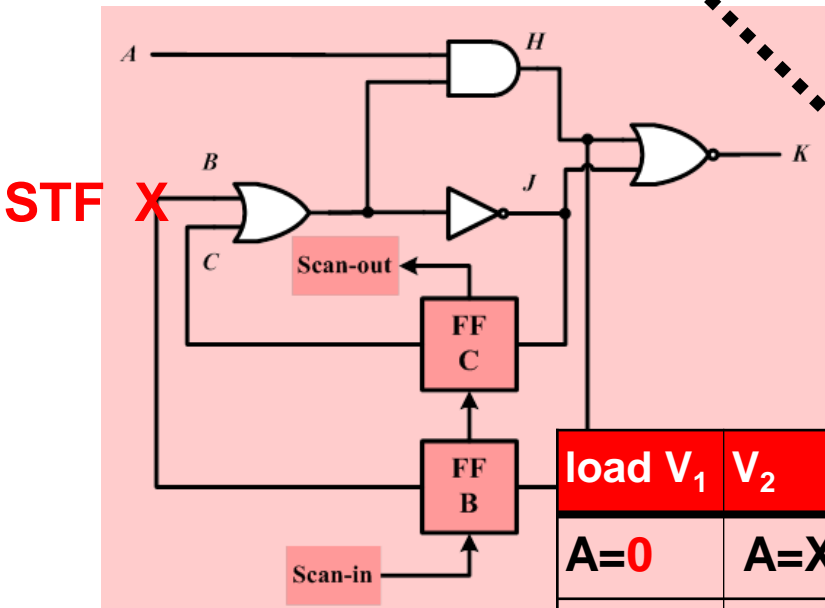


| load | V ₁ | V ₂ | capture | unload |
|-------|----------------|----------------|---------|--------|
| A=0 | | A=X | K=X | |
| SI=X1 | | | | SO=HX |

Quiz

Q1: Please draw ckt model for LOC

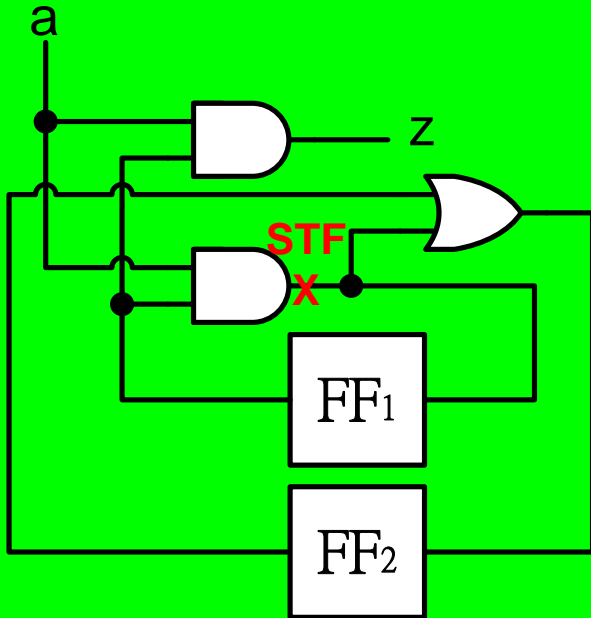Q2: Generate LOC test pattern for STF fault.







Summary

- Run comb. ATPG on seq. ckt with DFT
- SSF: All FF becomes PPI/PPO
- LOS
 - ♦ Generate V_2 first, then add constraints to V_1
 - 😊 Small memory. Fast run time
 - 😞 **Fault coverage limited** due to structural dependency problem
- LOC
 - ♦ Duplicate Ckt into two copies
 - 😊 Good FC
 - 😞 **More memory. Slow run time**
- Current practice: mix LOS and LOC
 - ♦ Do **LOS first**, save memory/computation time
 - ♦ **Then do LOC**, detect remaining faults

FFT

- Q: In LOS ATPG, why generate V_2 first? Why not V_1 first?
 - ♦ 1. Generate SSF pattern for V_2 ,
 - ♦ 2. Apply constraints to generate V_1

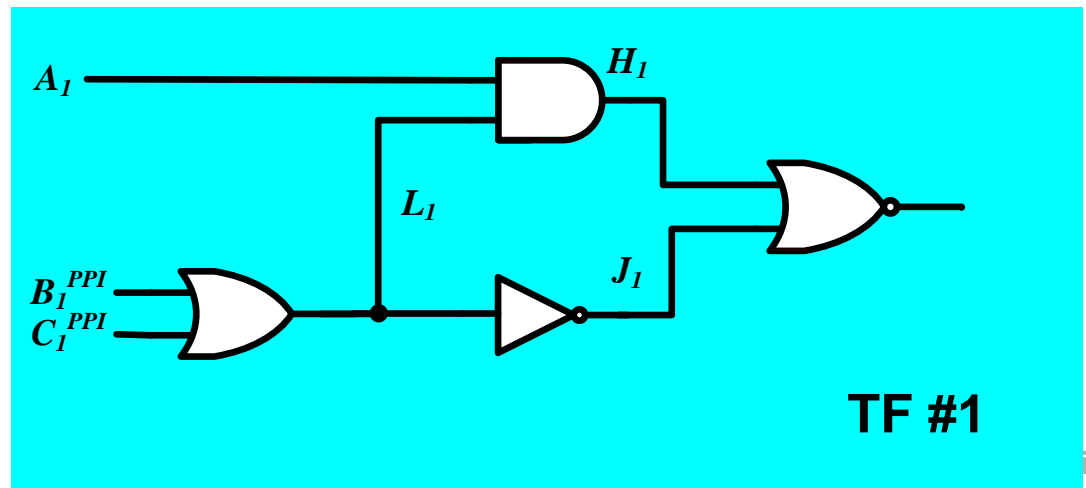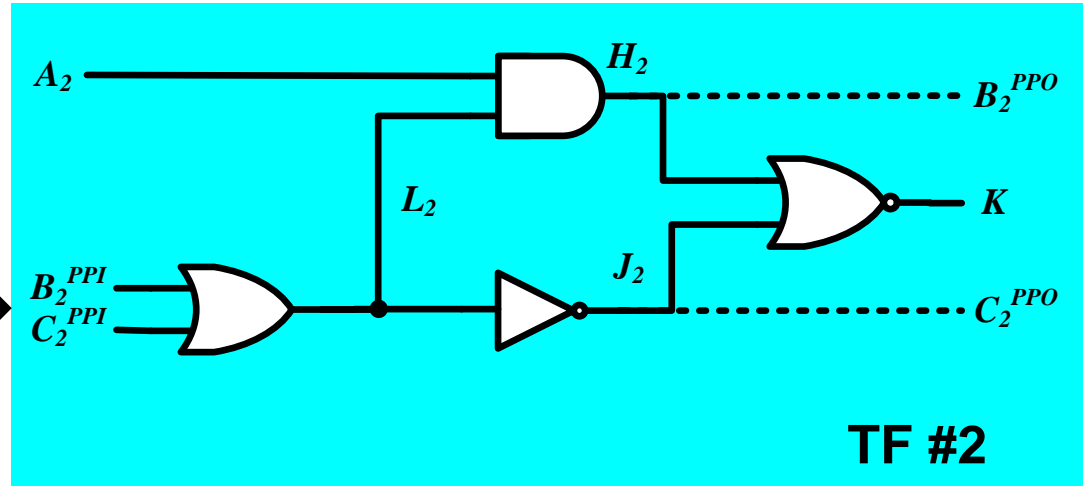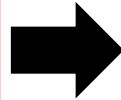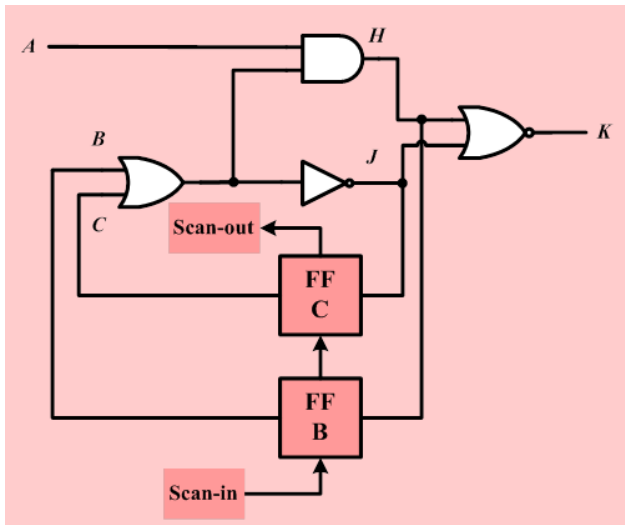

FFT 2

**Q: This model assumes FF are good.
What if FF are faulty?**

