 



DFT - Part 1

- Introduction
- Internal Scan
 - ◆ FF-based
 - * MUXed-D scan (1973, Stanford)
 - * Clocked scan (1968, NEC)
 - * Other scan
 - ◆ Latch-based
 - * LSSD (1977, IBM)
- Scan Design Flow
- Issues and Solutions
- Conclusion



Level Sensitive Scan Design, LSSD

 - Invented by IBM [Eichelberger 77]
- Master-slave latch
 - ♦ Master L_1 : 2-port latch, **AC** clocks
 - ♦ Slave L_2 : 1-port latch, **B** clock
 - ♦ 2 inputs: Data input (**D**); Scan input (**I**)
 - ♦ 2 outputs: **+L1**, **+L2**




LSSD scan latch is called:
Shift Register Latch (SRL)


Normal Mode Operation

- **Clocking sequence:**

 - ◆ **C clock B clock: $D \rightarrow +L_1 \rightarrow +L_2$**




(WWW Fig. 2.12)

 

Double Latch-based Design (w/o LSSD)

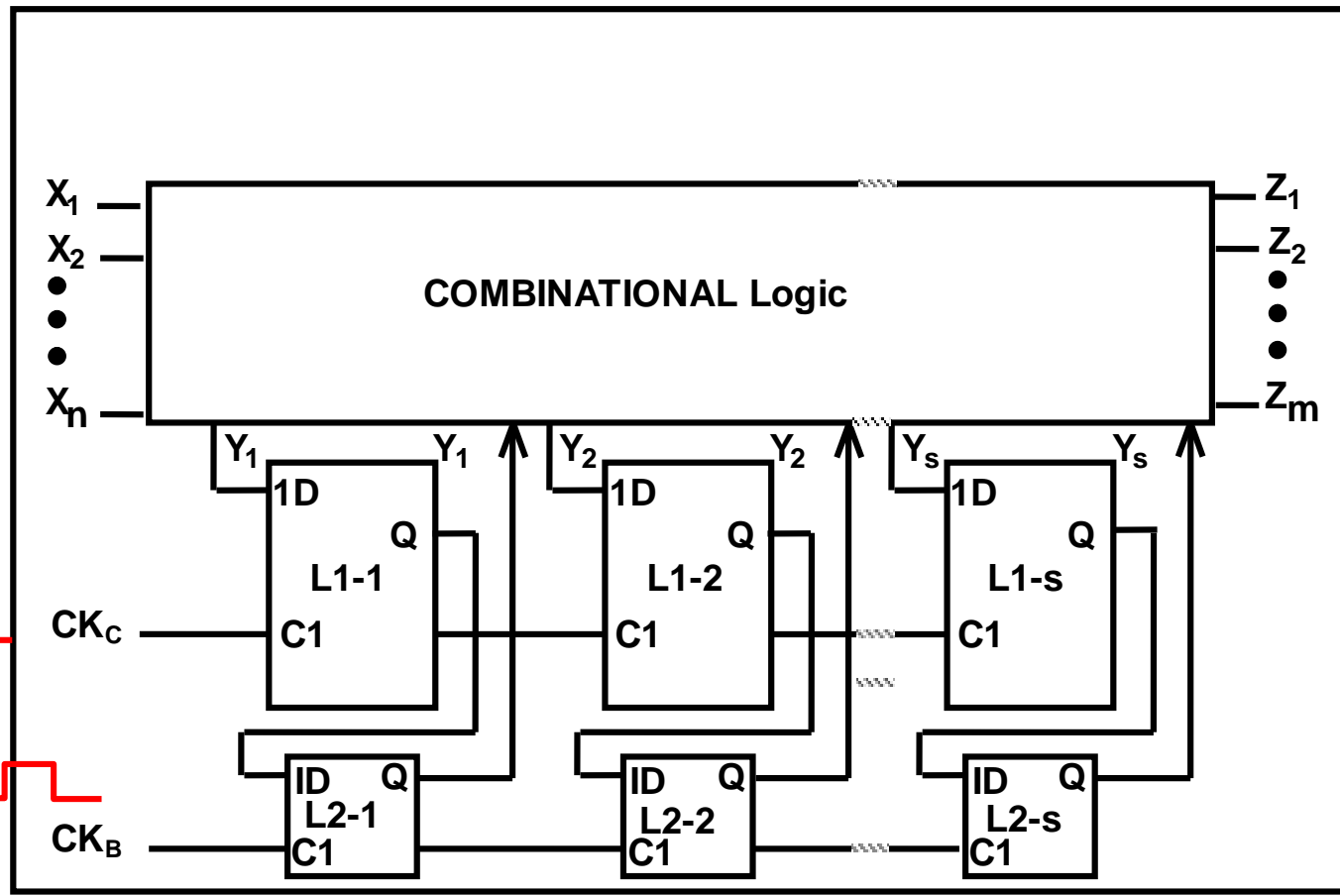
- Normal operation mode: CK_C CK_B , CK_C CK_B ...
 - ♦ Clock B and C non-overlapping



(Courtesy of Prof. McCluskey, Stanford)

Another Point of View

 
- 2 latches per stage: L1 and L2
- Normal mode: CK_C CK_B , CK_C CK_B ...
 - ♦ non-overlapping clocks, avoid clock skew




Shift

- **Clocking sequence:**

 - ◆ **A clock B clock: $I \rightarrow +L_1 \rightarrow +L_2$**




(WWW Fig. 2.12)

 

Double Latch-based Design (w/ LSSD)

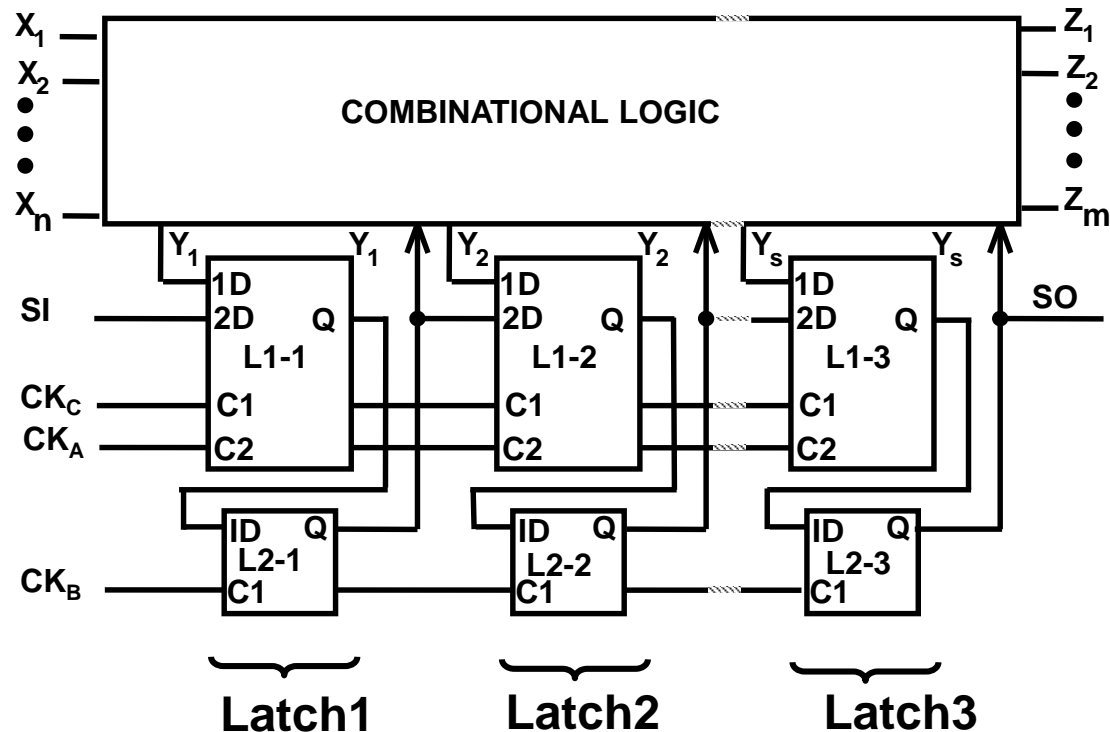- Replace L_1 1-port latch by **2-port latch**
- Add scan input (**SI**), scan output (**SO**)
- Add **A** clock




- **One-pattern test**
 - ◆ **Shift:** $CK_A CK_B, CK_A CK_B, CK_A CK_B$
 - ◆ **Capture:** CK_C
 - ◆ **Shift:** $CK_B CK_A, CK_B CK_A, CK_B$



Test Mode Operation (2)

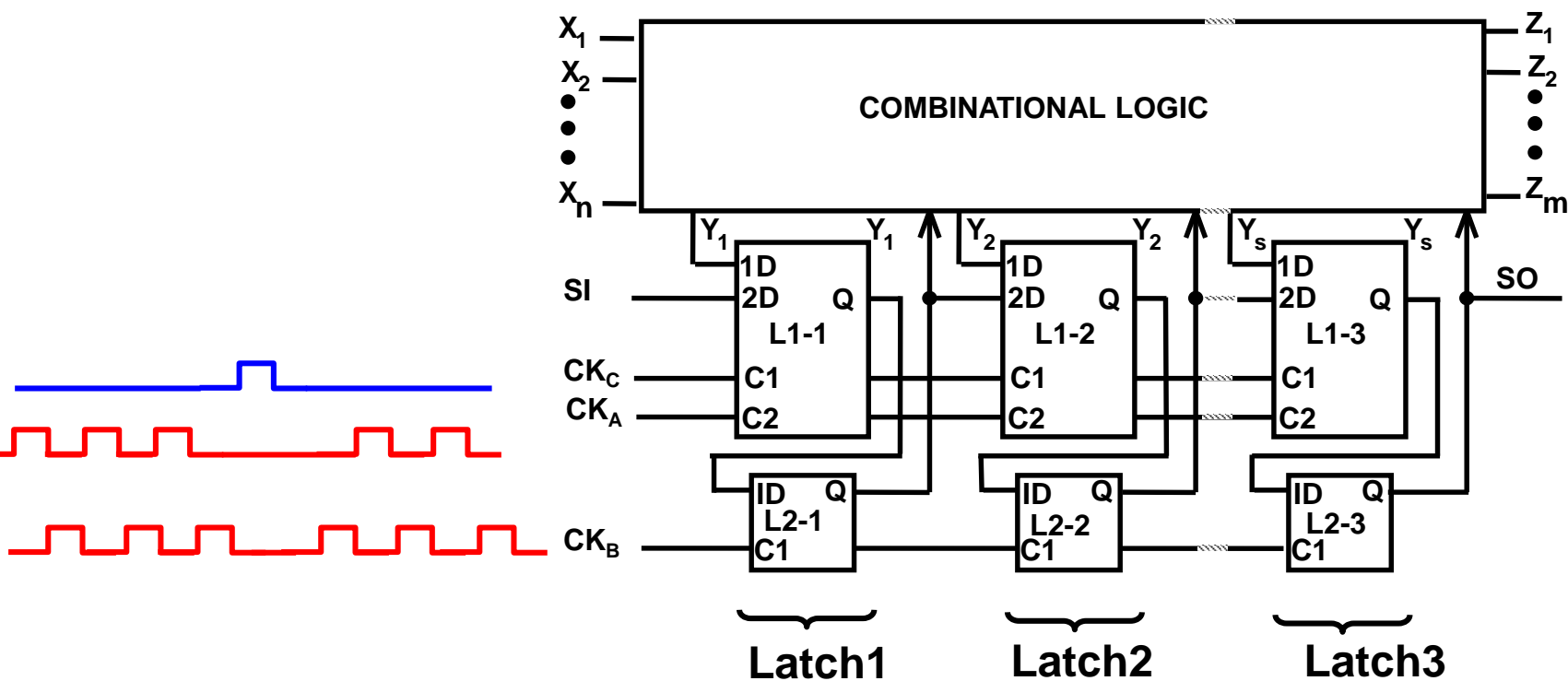- One-pattern test
 - ◆ Shift: $CK_A CK_B$, $CK_A CK_B$, $CK_A CK_B$
 - ◆ Capture: CK_C
 - ◆ Shift: $CK_B CK_A$, $CK_B CK_A$, CK_B




Summary of Three Internal Scans

- **LSSD**
 - ◆ 😊 No clock skew
 - ◆ popular for latch-based design
- **Muxed D-Scan**
 - ◆ 😊 Very popular for FF-based design
 - ◆ 😞 Speed degradation: one MUX delay (about 2 gate delay)
 - ◆ Adopted by most ASIC designs
- **Clock Scan**
 - ◆ 😊 Little speed degradation
 - ◆ 😞 Need extra clock routing for SCK
 - ◆ Adopted by advanced designs

FFT

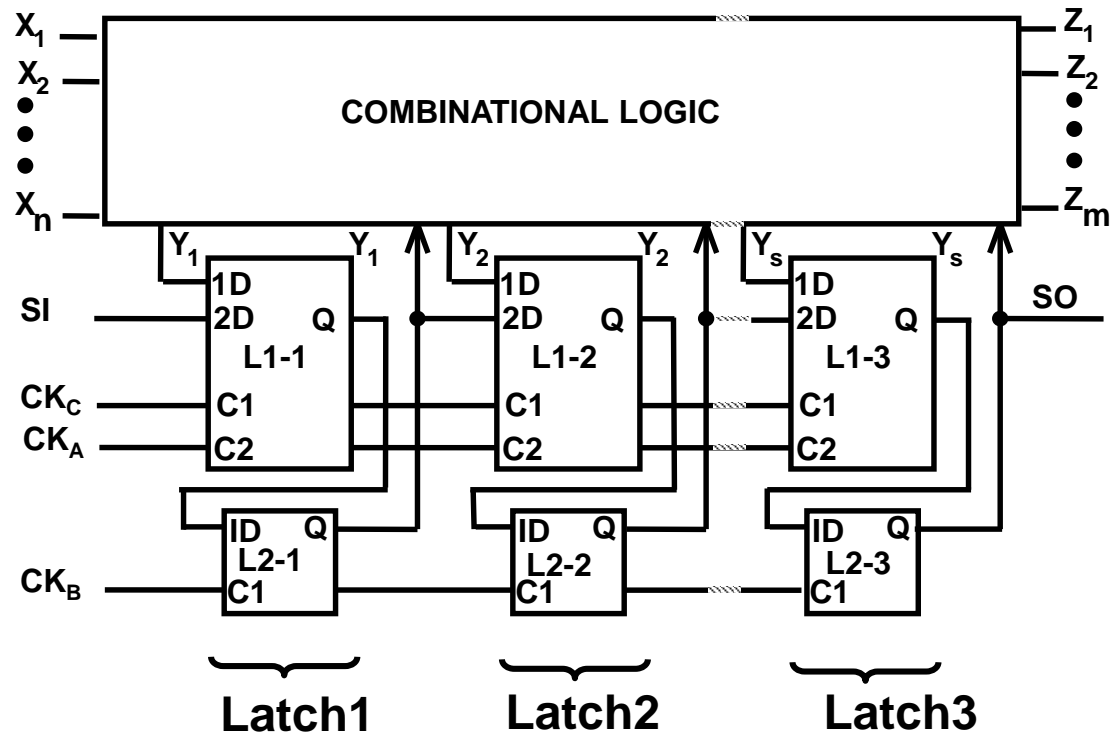- Q: how to apply 2-pattern test for LSSD?



?